



APPLICATION BULLETIN

Mailing Address: PO Box 11400 • Tucson, AZ 85734 • Street Address: 6730 S. Tucson Blvd. • Tucson, AZ 85706
Tel: (602) 746-1111 • Twx: 910-952-111 • Telex: 066-6491 • FAX (602) 889-1510 • Immediate Product Info: (800) 548-6132

IMPLEMENTATION AND APPLICATIONS OF CURRENT SOURCES AND CURRENT RECEIVERS

This application guide is intended as a source book for the design and application of:

- Current sources
- Current sinks
- Floating current sources
- Voltage-to-current converters (transconductance amplifiers)
- Current-to-current converters (current mirrors)
- Current-to-voltage converters (transimpedance amplifiers)

This is not an exhaustive collection of circuits, but a compendium of preferred ones. Where appropriate, suggested part numbers and component values are given. Where added components may be needed for stability, they are shown. Experienced designers may elect to omit these components in some applications, but less seasoned practitioners will be able to put together a working circuit free from the frustration of how to make it stable.

The applications shown are intended to inspire the imagination of designers who will move beyond the scope of this work.

R. Mark Stitt (602) 746-7445

CONTENTS

DESIGN OF FIXED CURRENT SOURCES

REF200 IC CURRENT SOURCE
DESCRIPTION, PIN STRAPPING REF200 FOR 50 μ A—400 μ A .. 2

RESISTOR PROGRAMMABLE CURRENT SOURCES
AND SINKS USING REF200 AND ONE EXTERNAL OP AMP:
Current Source or Sink With Compliance to
Power Supply Rail and Current Out >100 μ A 4
Current Source or Sink With Any Current Out 5
Floating Current Source With Current Out >100 μ A 5
Current Sources made with Voltage References 5
Current Sources and Sinks and Current Mirrors
Using an Amplifier and a Series Pass Element 6
Floating Current Source With
Current Out >100 μ A and No Separate Power Supply 6

CASCODING CURRENT SOURCES
FOR IMPROVED OUTPUT IMPEDANCE,
HIGH FREQUENCY PERFORMANCE,
AND HIGH VOLTAGE COMPLIANCE:
Cascoding with FETs 8
200 μ A Floating Cascoded Current Source Using REF200 ... 9
300 μ A Floating Cascoded Current Source Using REF200 . 10
400 μ A Floating Cascoded Current Source Using REF200 . 10

NOISE REDUCTION OF CURRENT SOURCES 10

APPLICATIONS OF FIXED CURRENT SOURCES

VOLTAGE REFERENCES USING CURRENT SOURCES 11
OP AMP OFFSET
ADJUSTMENT USING 5mV REFERENCE 12
WINDOW COMPARATOR USING
FLOATING VOLTAGE REFERENCE 13
RTD EXCITATION USING CURRENT REFERENCE 13

DEAD BAND CIRCUITS USING CURRENT REFERENCE 14
BIDIRECTIONAL CURRENT SOURCES 16

LIMITING CIRCUITS USING
BIDIRECTIONAL CURRENT SOURCES 16
PRECISION TRIANGLE WAVEFORM GENERATOR
USING BIDIRECTIONAL CURRENT SOURCES 17
DUTY CYCLE MODULATOR USING
BIDIRECTIONAL CURRENT SOURCES 17
SLEW RATE LIMITER 18
SINGLE SUPPLY INSTRUMENTATION AMPLIFIER 18

VOLTAGE CONTROLLED CURRENT SOURCES

VOLTAGE CONTROLLED
CURRENT SOURCE USING INA105 18
VOLTAGE CONTROLLED CURRENT SOURCE WITH
INSTRUMENTATION AMPLIFIER INPUT—THE XTR101 20
SINGLE SUPPLY VOLTAGE
CONTROLLED CURRENT SOURCE—THE XTR110 20

CURRENT-TO-VOLTAGE CONVERTERS, AND CURRENT RECEIVERS

CURRENT RECEIVER WITH COMPLIANCE TO
BOTH POWER SUPPLY RAILS USING THE INA105 22
POWER AMP LOAD CURRENT
MONITORING USING THE INA105 OR THE INA117 22
4 to 20mA CURRENT LOOP RECEIVER
WITH 0 to 5V OUTPUT USES THE RCV420 23
VIRTUAL GROUND CURRENT
TO VOLTAGE CONVERTER 23
PHOTODIODE AMPLIFIERS 23

GLOSSARY 27

DESIGN OF FIXED CURRENT SOURCES

REF200 IC CURRENT SOURCE DESCRIPTION

The REF200 dual current source has two current sources plus a current mirror in an 8-pin plastic DIP (Figure 1). Because the circuit is fabricated with the Burr-Brown dielectrically isolated **Difet**® Burr-Brown process, the three circuit blocks are completely independent. No power supply connections are needed to the chip. Just apply 2.5V or more to a current source for a constant 100μA output. Typical drift is less than 25ppm/°C and output impedance exceeds 500MΩ.

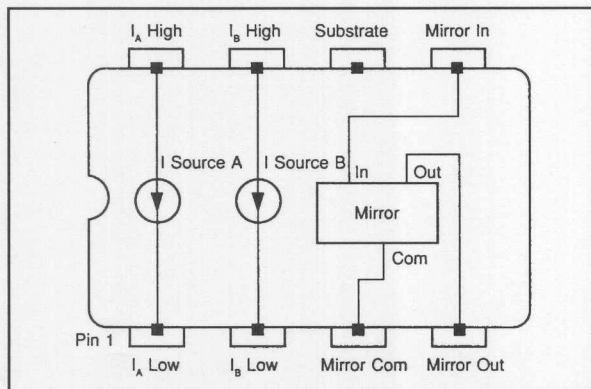


FIGURE 1. The REF200 Dual Current Source contains three completely independent circuit blocks—two 100μA current sources, and a current mirror.

The current mirror is useful in many applications. It uses a “full Wilson” type architecture as shown in Figure 2, with laser-trimming to ensure high accuracy.

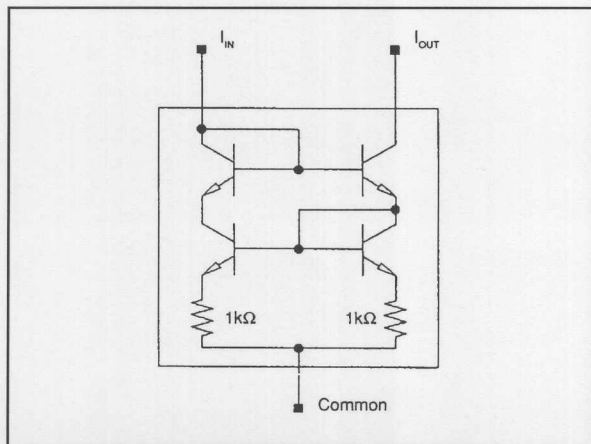


FIGURE 2. The REF200 Current Mirror uses a “full Wilson” architecture for high accuracy.

Each of the two current sources are designed as shown in Figure 3. Zero temperature coefficient (TC) is achieved by combining positive TC currents with a negative TC current. The positive TC currents are generated by a bandgap cell.

Current mirror $Q_1 - Q_2$ forces equal currents to flow in 8/1 emitter ratioed devices Q_7 and Q_8 . The proportional to absolute temperature (PTAT) voltage difference between the emitters— $(k \cdot t/q) \cdot \ln(8)$ —is forced across the 4kΩ resistor resulting in a PTAT current of about 13μA. Because Q_{10} matches Q_7 , and Q_3 matches Q_4 , equal PTAT currents flow in each of the four $Q_1 - Q_4$ legs. The current in the Q_4 leg biases a $V_{be}/12kΩ$ current generator formed by Q_{11} and Q_{12} . The negative TC current from Q_{11} sums at the output. The 4kΩ and 12kΩ resistors are actively laser trimmed over temperature at wafer level to give an accurate zero TC output. NPN transistors Q_5 , Q_6 , and Q_9 cascode Q_7 and Q_8 for improved accuracy and output impedance. Likewise, J_1 and J_2 cascode Q_3 and Q_4 . Using FET cascodes rather than PNPs eliminates noise due to base current. The capacitor provides loop compensation.

100μA was chosen as a practical value for the majority of applications. It is high enough to be used directly for sensor excitation in many instances, while it is low enough to be used in low power and battery powered applications where a higher current might be excessive. Also at higher output currents, thermal feedback on the chip and self heating would reduce the output impedance.

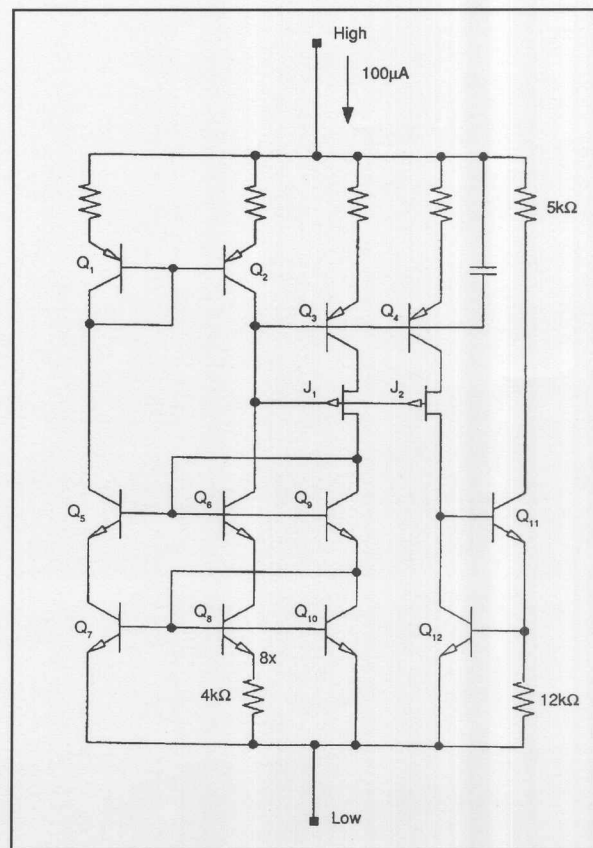


FIGURE 3. The REF200 Current Source cell is powered from its input terminals. It achieves zero TC by summing a positive TC current from a bandgap cell with a negative TC current.

Difet® Burr-Brown Corp.

PIN STRAPPING REF200 FOR: 50 μ A CURRENT SINK

With a 100 μ A current source as a reference, it is simple to construct a current source of any value. The REF200 can be pin strapped for 50 μ A, 200 μ A, 300 μ A, or 400 μ A, in addition to 100 μ A.

For a 50 μ A current sink, use the circuit shown in Figure 4. A 100 μ A current source is tied to the mirror common. Since a current mirror output must equal its input, 50 μ A flows in the input to ground, and the output is a 50 μ A current sink.

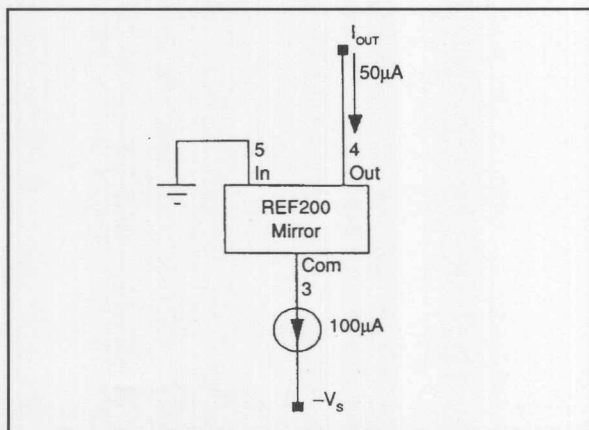


FIGURE 4. A 50 μ A Current Sink with compliance to ground can be made using one of the 100 μ A current sources and the mirror from the REF200.

PIN STRAPPING REF200 FOR: 50 μ A Current Source

For a 50 μ A current source, use the circuit shown in Figure 5. In this circuit a current sink subtracts 50 μ A from a second 100 μ A source leaving a 50 μ A source. Compliance is from below ground to within 2.5V of the positive rail.

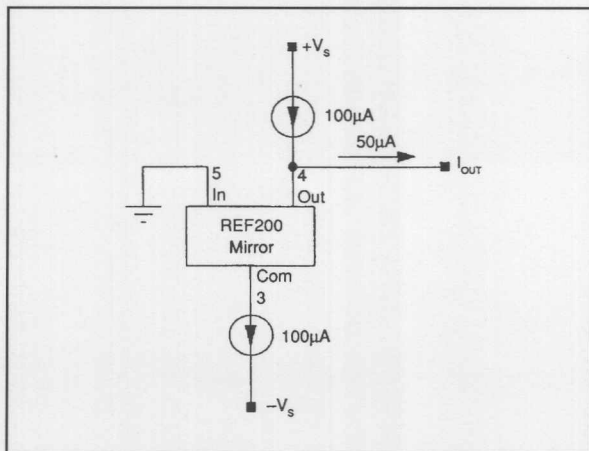


FIGURE 5. A 50 μ A Current Source with compliance from ground to $+V_s - 2.5V$ can be made using both 100 μ A current sources and the mirror from the REF200.

If compliance closer to the negative rail is needed for either the 50 μ A sink or source, use the circuit shown in Figure 6, or Figure 7. Here the mirror input is referenced to the negative rail with either a resistor and current source, or a resistor biased zener.

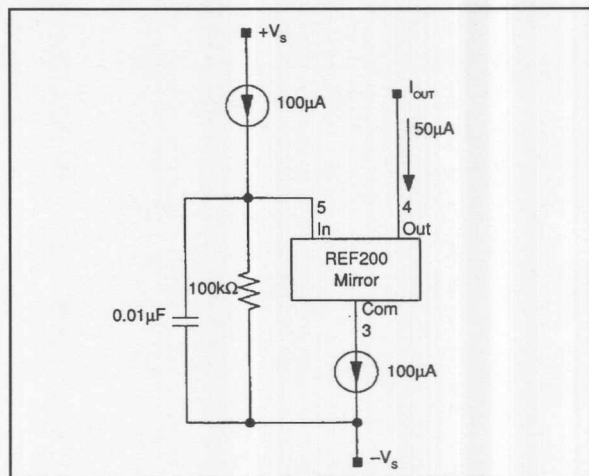


FIGURE 6. Compliance of the 50 μ A Current Sink (Figure 5) can be extended to $-V_s + 5V$ by referencing its bias point to the negative power supply rail using the other 100 μ A current and a resistor.

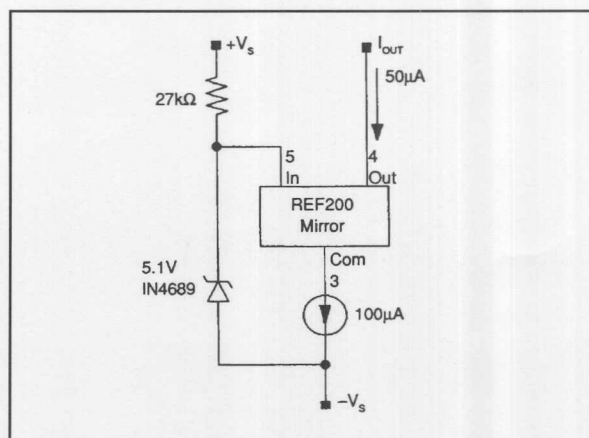


FIGURE 7. If you don't have a current source to spare, the 50 μ A Current Sink with compliance to $-V_s + 5V$ can be biased using a zener diode.

PIN STRAPPING REF200 FOR: 200 μ A FLOATING CURRENT SOURCE

A 200 μ A floating current source is formed by simply paralleling the two current sources as shown in Figure 8. For compliance nearer to the negative rail, use the mirror as shown in Figure 9. The output of the mirror can swing about a volt closer to the negative rail than the current source alone.

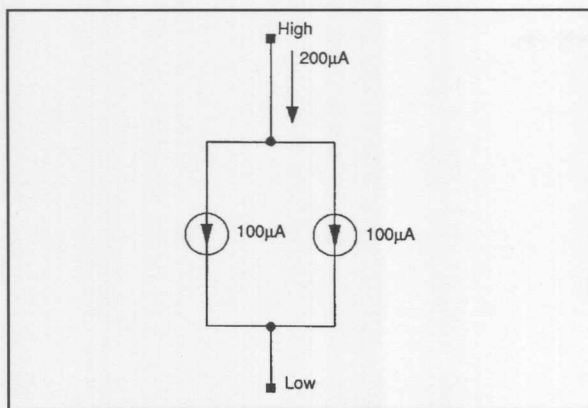


FIGURE 8. For a 200µA Floating Current Source simply parallel the two 100µA current sources from the REF200.

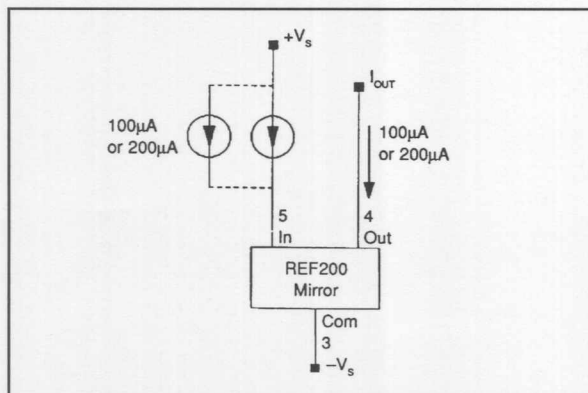


FIGURE 9. You can mirror the 100µA or 200µA Current Sources from the REF200 for a 100µA or 200µA current sink with improved compliance.

PIN STRAPPING REF200 FOR: 300µA Floating Current Source

A 300µA floating current source can be strapped together as shown in Figure 10. It is formed by paralleling a 200µA current source, made with one 100µA source and the mirror, with the other 100µA current source. The 200µA current source is made by connecting a 100µA current source to the mirror input so 100µA flows in the mirror output, and 200µA flows in the mirror common.

PIN STRAPPING REF200 FOR: 400µA Floating Current Source

A 400µA floating current source can be strapped together as shown in Figure 11. It is basically the same as the 200µA current source of Figure 10, except that 200µA is fed into the mirror input. This 200µA is summed with the 200µA that flows in the mirror output for a total of 400µA.

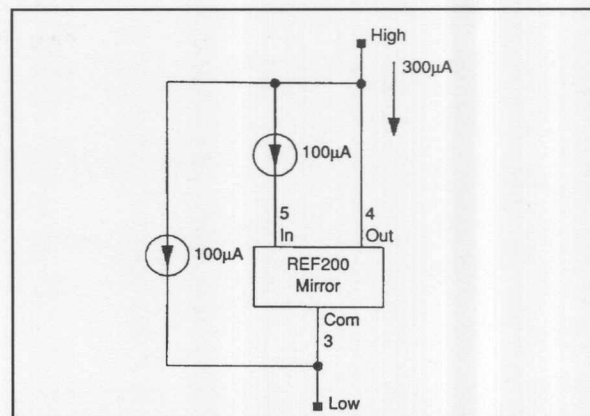


FIGURE 10. The two 100µA Current Sources and Mirror in the REF200 can be connected to form a 300µA floating current source.

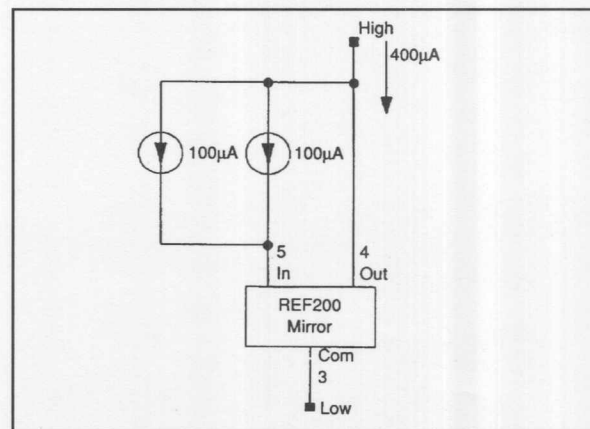


FIGURE 11. The two 100µA Current Sources and Mirror in the REF200 can be connected to form a 400µA floating current source.

RESISTOR PROGRAMMABLE CURRENT SOURCES AND SINKS USING REF200 AND ONE EXTERNAL OP AMP:

Current Source or Sink With Compliance to Power Supply Rail and Current Out >100µA

You can build a programmable current source of virtually any value using two resistors, an op amp, and a 100µA current source as a reference.

The current source shown in Figure 12 can be programmed to any value above the 100µA reference current. It has compliance all the way to the negative power supply rail. The 100µA reference forces a voltage of $100\mu\text{A} \cdot R_1$ at the non-inverting input of the op amp. When using a *Difet*® op amp as shown, input bias currents are negligible. The op amp forces the same voltage across R_2 . If R_1 is $N \cdot R_2$, the output current is $(N+1) \cdot 100\mu\text{A}$. So long as the op amp input common mode range and its output can swing to the negative rail within the voltage drop across R_1 , the current source can swing all the way to the negative rail. If the voltage drop across R_1 is large enough, any op amp can

satisfy this requirement. Figure 13 shows the same circuit turned around to act as a current sink. It has compliance to the positive rail.

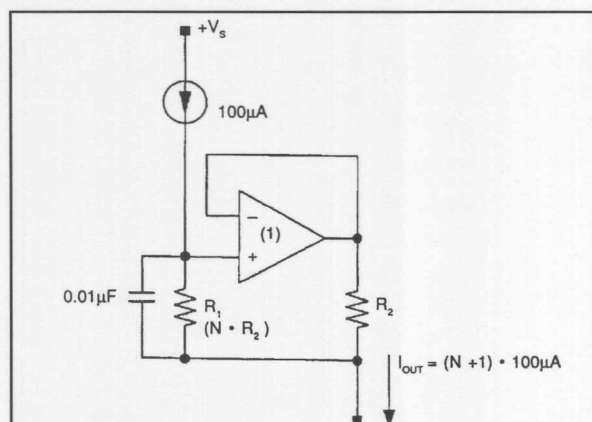


FIGURE 12. Current Source.

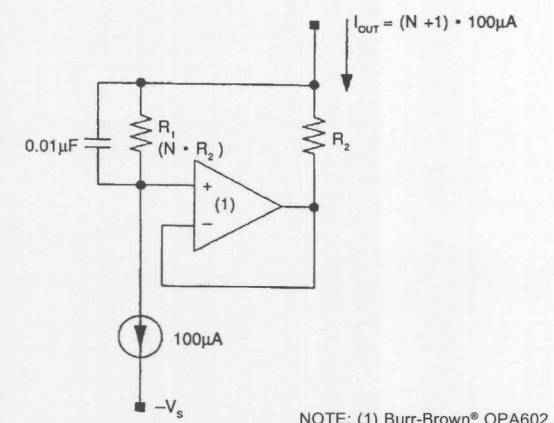


FIGURE 13. Current Sink.

FIGURES 12 and 13. For a programmable current source with any output current greater than $100\mu\text{A}$ and compliance to $+V_s$ or $-V_s$, use a $100\mu\text{A}$ current source as a reference along with an external op amp and two programming resistors.

Current Source or Sink With Any Current Out

For currents less than $100\mu\text{A}$, use the circuits shown in Figures 14 and 15. They can be programmed for virtually any current (either above or below $100\mu\text{A}$). In this case the $100\mu\text{A}$ current source forms a reference across R_1 at the inverting input of the op amp. Since the reference is not connected to the output, its current does not add to the current output signal. So, if R_1 is $N \cdot R_2$, then output current is $N \cdot 100\mu\text{A}$. Because compliance of the $100\mu\text{A}$ current source is 2.5V , the current source, Figure 14, can only comply within 2.5V of the negative rail—even if the op amp can go further. Likewise the current sink, Figure 15, has a 2.5V compliance to the positive power supply rail.


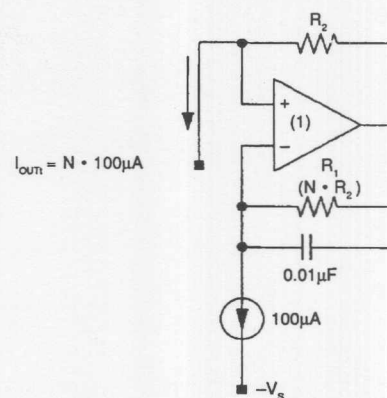


FIGURE 14. Current Source.

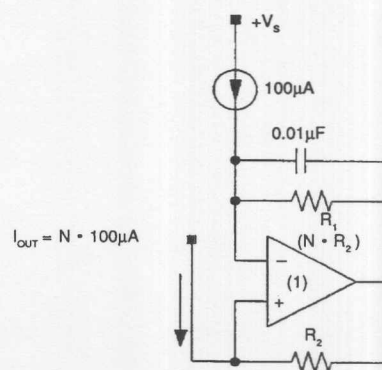

NOTE: (1) Burr-Brown® OPA602 or OPA128.

EXAMPLES

R_1	R_2	I_{OUT}	
100Ω	$10\text{M}\Omega$	1nA	→ Use OPA128
$10\text{k}\Omega$	$1\text{M}\Omega$	$1\mu\text{A}$	
$10\text{k}\Omega$	$1\text{k}\Omega$	1mA	

FIGURES 14 and 15. If you don't need compliance to the power supply rail, this circuit using a $100\mu\text{A}$ current source as a reference along with an external op amp and two programming resistors can provide virtually any output current.

Current Sources and Sinks Using Voltage References

To make a current source with the best possible accuracy use a zener-based voltage reference. The REF200 uses a band-gap type reference to allow low voltage two-terminal operation. Although this makes a more flexible general-purpose part with excellent performance, its ultimate temperature drift and stability cannot compare to the REF102 precision 10.0V buried zener voltage reference.

Make a current source from a voltage reference using the circuit shown in Figure 15A. The voltage follower connected op amp forces the voltage reference ground connection to be equal to the load voltage. The reference output then forces an accurate 10.0V across R_1 so that the current source output is $10V/R_1$.

Negative output compliance for the current source is limited by the op amp input common-mode range or output range (whichever is worse). When using the OPA111 on $\pm 15V$ power supplies, the negative compliance is $-10V$. For compliance almost to the negative power supply rail, use a single-supply op amp such as the OPA1013.

Positive output compliance is limited by the voltage reference minimum $+V_s$ requirement. When using the REF102 on $\pm 15V$ power supplies, positive compliance is $+3.5V$.

Make a current sink with a voltage reference using the circuit shown in Figure 15B. The op amp drives both the voltage reference ground connection and the current scaling register, R_1 , so that the voltage reference output is equal to the load voltage. This forces $-10.0V$ across R_1 so that the current sink output is $-10V/R_1$. The R_2 , C_1 network provides local feedback around the op amp to assure loop stability. It also provides noise filtering. With the values shown, the reference noise is filtered by a single pole with $f_{-3dB} = 1/(2 \cdot \pi \cdot R_2 \cdot C_1)$.

Negative output compliance for the current sink is limited by the op amp and further reduced by the 10V drop across R_1 . When using the OPA111 on $\pm 15V$ power supplies, negative compliance is only guaranteed to ground. When using the single-supply OPA1013 op amp, negative compliance is approximately $-5V$.

Positive compliance is limited by the REF102, but is improved by the 10V across R_1 . For a REF102 operating on $\pm 15V$ power supplies, the positive compliance is $+10V$ (limited by the op amp common mode input range).

Keep in mind that the ultimate accuracy of a voltage reference based current source depends on the absolute accuracy of the current-scaling resistor. The absolute TCR and stability of the resistor directly affect the current source temperature drift and accuracy. This is in contrast to circuits using current source references, as shown in Figures 12 to 15, where accuracy depends only on the ratio accuracy of the resistors. It is much easier to get good resistor ratio accuracy than to get good absolute accuracy especially when using resistor networks.

Although these current sources made with voltage references do not have the compliance range of the previous circuits, they may be the best choice where the utmost in accuracy is required.

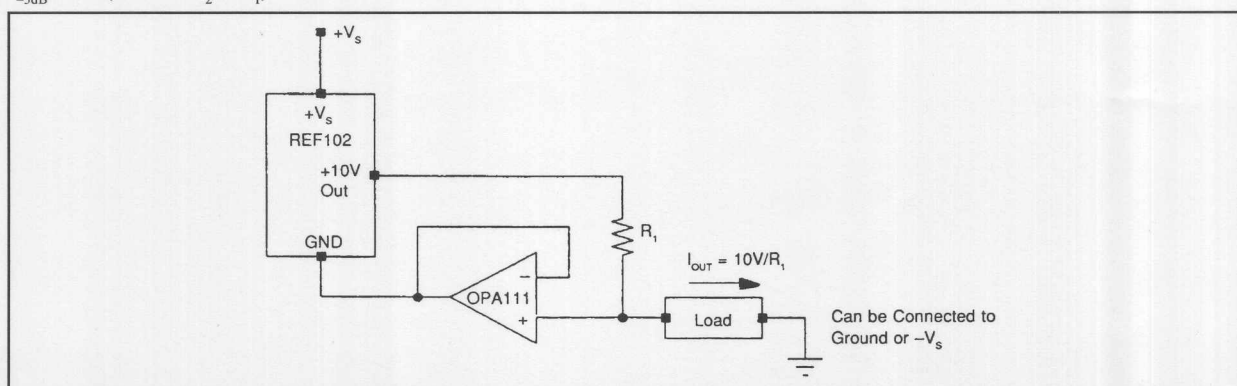


FIGURE 15A. Current Source using Voltage Reference and Op Amp.

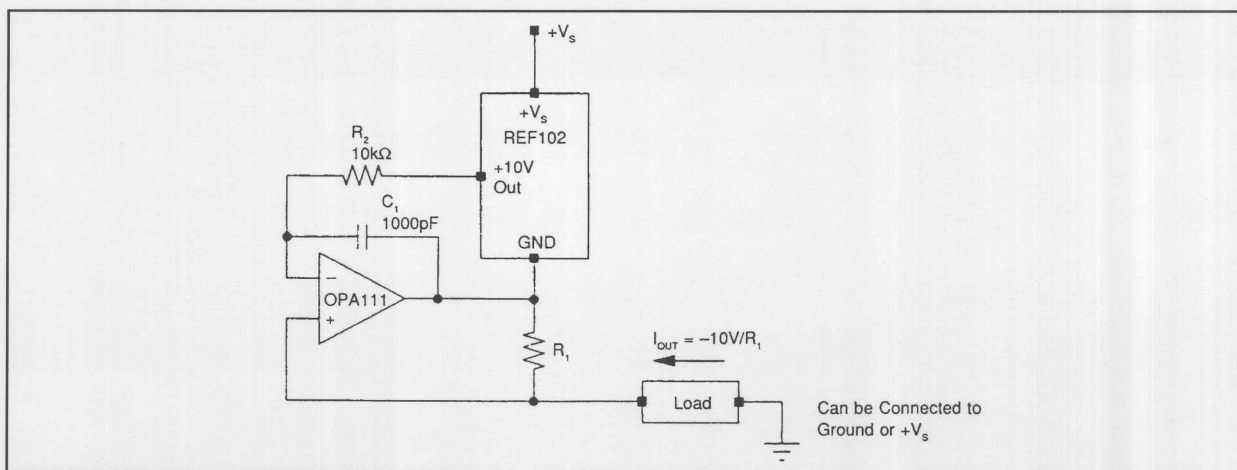


FIGURE 15B. Current Sink using Voltage Reference and Op Amp.

Floating Current Source With Current Out > 100 μ A

If a completely floating programmable current source is needed, use the circuit shown in Figure 16. It is basically the same as the current source shown in Figure 12 except that R_2 is driven by a MOSFET. Since no current flows in the gate of the MOSFET or the inputs of the op amp, all current that enters the resistors (and no more) leaves. Therefore the current source is completely floating.

The power supplies of the op amp in this circuit, as in the other circuits, must be connected to $\pm V_s$. Also, the input and output common mode limitations of the op amp must be observed.

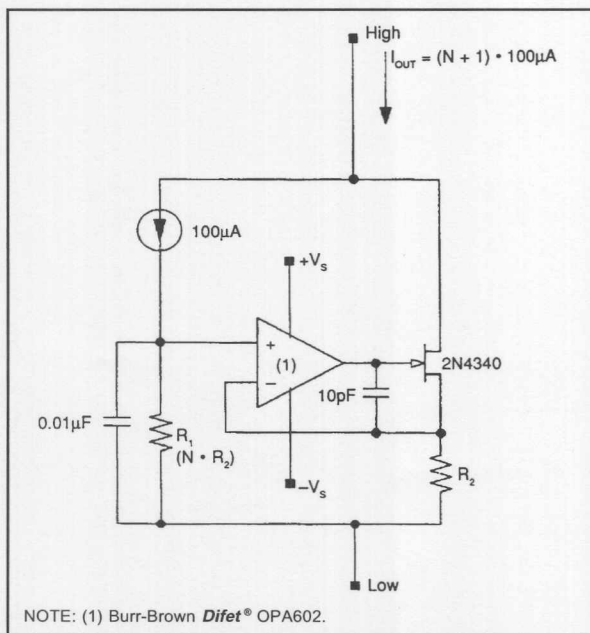


FIGURE 16. Use a 100 μ A Current Source as a reference, an external op amp, two programming resistors, and a series pass element for a programmable floating current source.

Current Sources and Sinks and Current Mirrors Using an Amplifier and a Series Pass Element

In some applications it may be desirable to make a current source or sink using a series pass element in addition to an op amp. This approach provides the benefits of cascoding and also allows arbitrarily high current outputs.

The circuit used is the same as for the programmable floating current source shown in Figure 16. The difference is that the op amp power supply connection and reference input are both returned to a fixed potential. The result is either a current source or sink, but not a floating current source. The advantage is that the output can be any value, either more than, less than, or equal to the input reference. Also, a voltage source or even a variable voltage input can be used as a reference. The examples shown in Figures 17 through 20 show 100 μ A current sources used as references.

Notice that since a current source is used as a reference, the circuit can also be used as a precision current mirror. Unlike mirrors which use matched transistors, this mirror remains highly accurate no matter what the mirror ratio.

The pass element can bipolar, JFET, MOSFET, or a combination. The examples recommend MOSFETs because their low gate current minimizes output error. Also, MOSFETs with very high current ratings are available, and require no additional drivers.

In many cases bipolar devices are adequate and may be preferred due to their low cost and availability. With a bipolar device, the base current will add error to the output signal as discussed in the cascoding section. Using a darlington-connected bipolar device feeds the error current back into the signal path and reduces the error by the forward current gain (beta) of the input transistor.

In some high temperature applications, darlington-connected bipolar transistors may have lower error than FETs. As a rule of thumb, the gate current of a FET or MOSFET doubles for every 8 $^{\circ}$ C increase in temperature, whereas the beta of a bipolar device increases approximately 0.5%/ $^{\circ}$ C. Therefore, when operating at 125 $^{\circ}$ C, the gate current of a FET will be about 6000 times higher than at 25 $^{\circ}$ C, while the base current of the bipolar will be 1.5 times lower.

When selecting the op amp for this application, pay particular attention to input bias current, input common mode range, and output range.

The bias current of the op amp adds to the input current, and subtracts from the output current. For a 1:1 mirror application, the error is only the mismatch of bias currents or I_{OS} of the amplifier. For other ratios, assume that the error is equal to the full amplifier bias current. For most applications, the error will be negligible if a low bias current **Difet**® amplifier such as the Burr-Brown OPA602 is used. Its I_B is 1pA max.

Be sure to observe the input common mode range limit of the op amp. For example, when using the OPA602 in a current sink application, the voltage between the op amp negative supply and its input must be at least 4V. In a split power supply application, R_1 and R_2 can be connected to ground, and the op amp negative supply can be connected to -5V or -15V and there is no problem. In a single supply application, or when R_1 , R_2 , and the op amp's $-V_s$ are all connected to the negative power supply, a drop of at least 4V must be maintained across R_1 .

Using a single supply op amp allows the input common mode range to go to 0V. Especially in single supply current mirror applications, it is often desirable for the input and output to go to zero. The OPA1013 has an input common-mode range which extends to its negative power supply, and its output will swing within a few mV of the negative supply. Although the OPA1013 has bipolar inputs, its bias current is low enough for most applications.

Components R_3 , R_4 , and C_1 form a compensation network to assure amplifier stability when driving the highly capacitive inputs of some MOSFETs. In many applications they can be omitted.

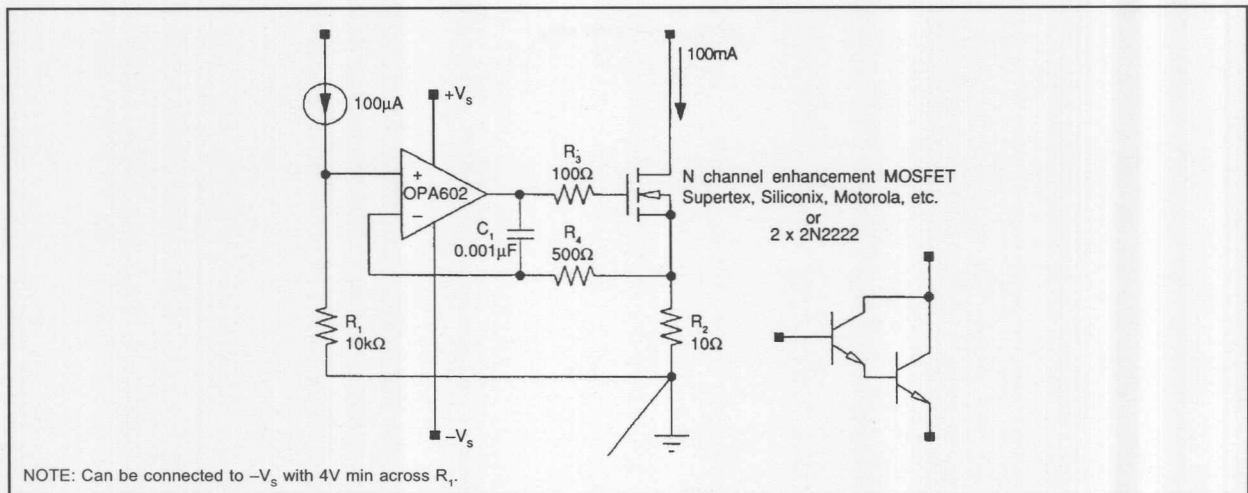


FIGURE 17. Programmable Current Sink using series pass device.

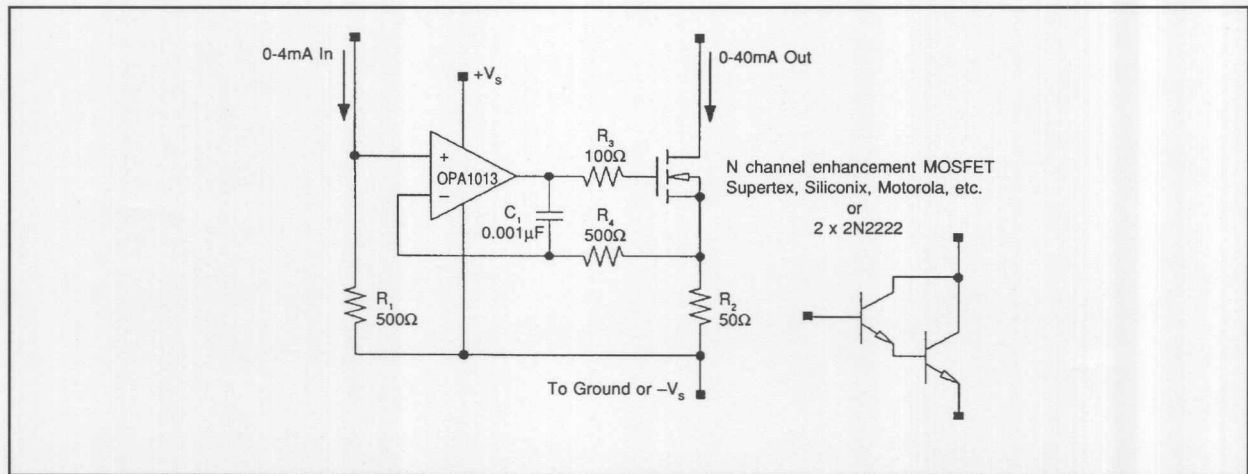


FIGURE 18. Sinking Current Mirror using series pass device.

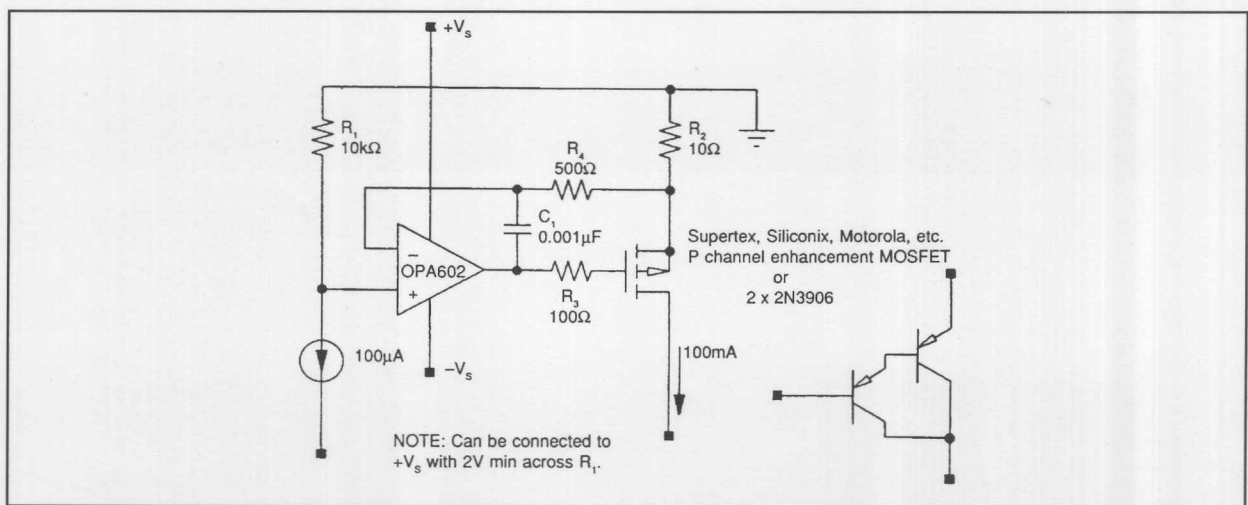


FIGURE 19. Programmable Current Source using series pass device.

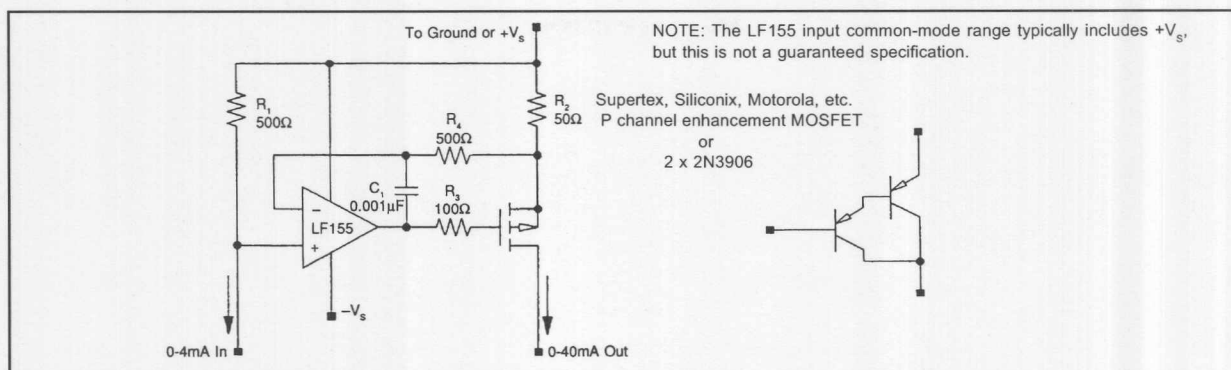


FIGURE 20. Sourcing Current Mirror using series pass device.

Floating Current Source With Current Out $>100\mu\text{A}$ and No Separate Power Supply

If a programmable current source is needed, and no separate power supply is available, consider the floating current source shown in Figure 21. Here the op amp power supplies are connected to the current source input terminals. The op amp quiescent current is part of the output current.

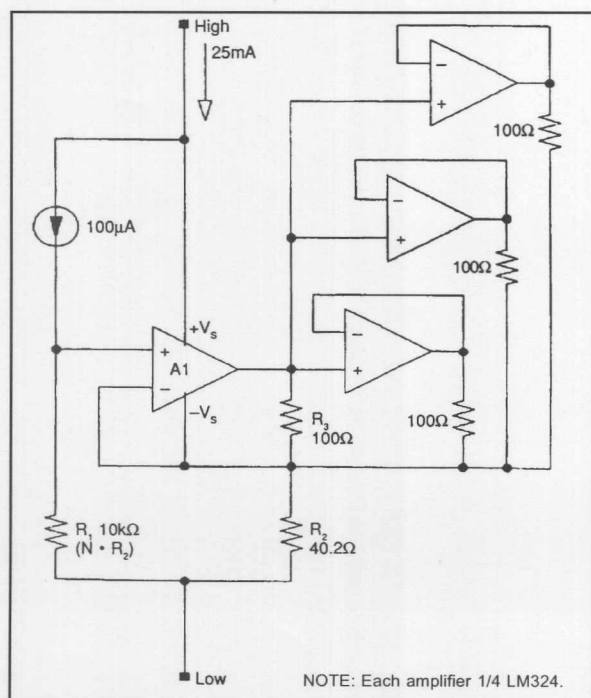


FIGURE 21. 25mA Floating Current Source using a quad single-supply op amp needs no external power supply.

There are two special requirements. First, a single supply op amp must be used (an op amp with an input common mode range that includes the negative supply rail). Also the output current must be greater than the op amp quiescent current.

The circuit is basically the same as Figure 12. The $100\mu\text{A}$ current flowing through R_1 produces a floating voltage reference at the non-inverting input of A_1 . The op amp

quiescent current flowing from its negative supply pin sums into the current flowing into R_2 . The op amp outputs drive the additional current needed through R_2 so the voltage drop across it matches the voltage drop across R_1 . If R_1 is $N \cdot R_2$, the output current is $(N+1) \cdot 100\mu\text{A}$. With the values shown, the output current is 25mA.

The op amp outputs are connected to R_2 through 100Ω resistors. The current delivered by A_1 produces an approximate $0.5V$ voltage drop across R_3 . The other three op amps are connected as voltage followers so that the same voltage is dropped across the other three 100Ω resistors. The output current from each op amp is therefore equal and the load is shared equally. This technique allows any number of $10mA$ output op amps to be paralleled for high output current.

CASCODING CURRENT SOURCES FOR IMPROVED OUTPUT IMPEDANCE, HIGH FREQUENCY PERFORMANCE, AND HIGH VOLTAGE COMPLIANCE

Cascoding With FETs

The output impedance and high frequency performance of any current source can be improved by cascoding. Starting with a precision current source like the REF200 or any of the variations previously discussed, it is relatively easy to build a current source to satisfy just about any need.

Cascoding can also be used to increase high voltage compliance. High voltage compliance of a cascoded current source is limited solely by the voltage rating of the cascoding device. High voltage compliance of hundreds or even thousands of volts is possible.

Cascoding is the buffering of the current source from the load by a series pass device as shown in Figure 22. Here an N channel JFET cascodes the current source from the output. The gate of the JFET is tied to ground, its source to the current source, and its drain to the load. Variations in the load voltage are taken up by the drain of the JFET while the source voltage remains relatively constant. In this way, the voltage drop across the current source remains constant regardless of voltage changes across the load. With no changes in the voltage across the current source, and with no current lost through the JFET drain approaches infinity. AC performance of the cascoded current sink approaches that of the JFET.

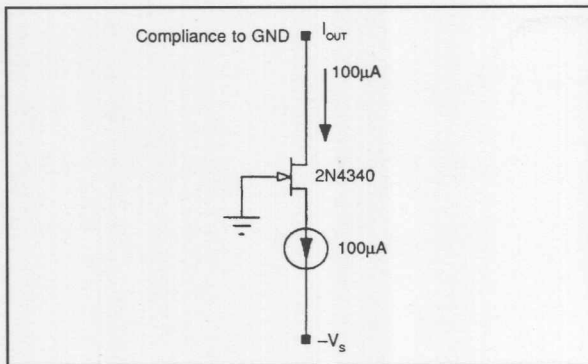


FIGURE 22. Cascoded Current Sink with compliance to ground.

Since the gate of the JFET is tied to ground, the output compliance is limited to near ground. If greater compliance is required for the current sink, the gate of the JFET can be referenced a few volts above the negative rail as shown in Figures 23 and 24. In Figure 23 the gate reference is derived from a resistor biased from the second current source. If a current source is not available, use a resistor biased zener as shown in Figure 24.

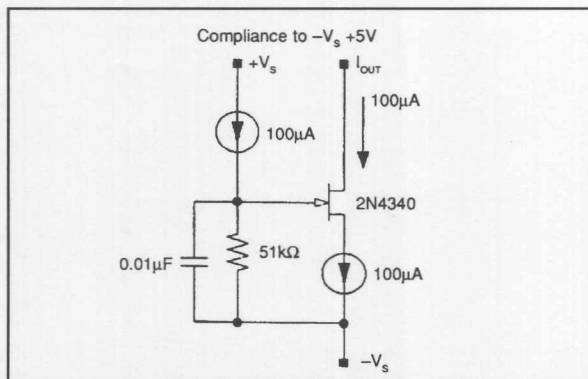


FIGURE 23. Cascoded Current Sink with compliance to $-V_S + 5V$ (using zener diode for bias).

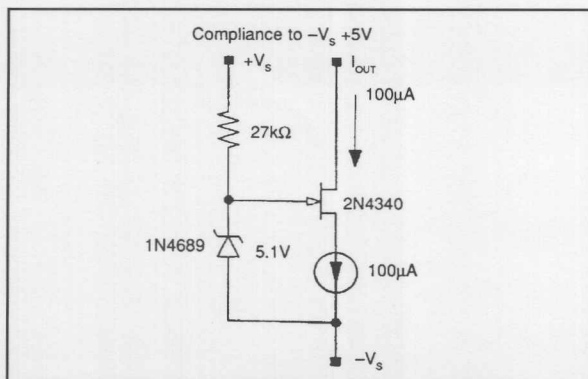


FIGURE 24. Cascoded Current Sink with compliance to $-V_S + 5V$ (using zener diode for bias).

To implement current sources, turn the circuits around and use P channel JFETs as shown in Figures 25 through 27.

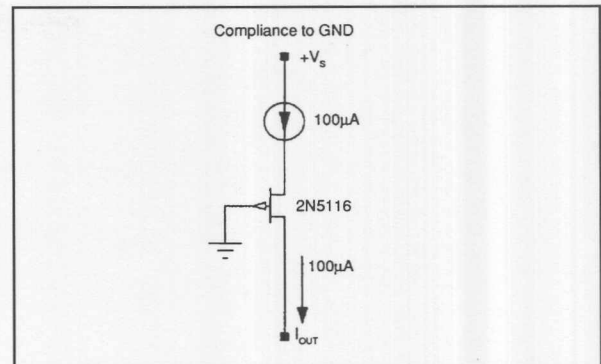


FIGURE 25. Cascoded Current Source with compliance to ground.

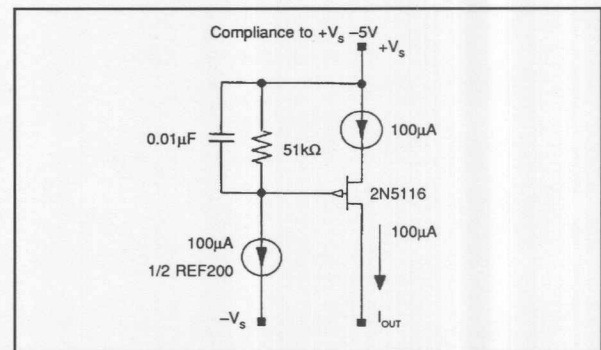


FIGURE 26. Cascoded Current Source with compliance to $-V_S + 5V$ (using current source and resistor for bias).

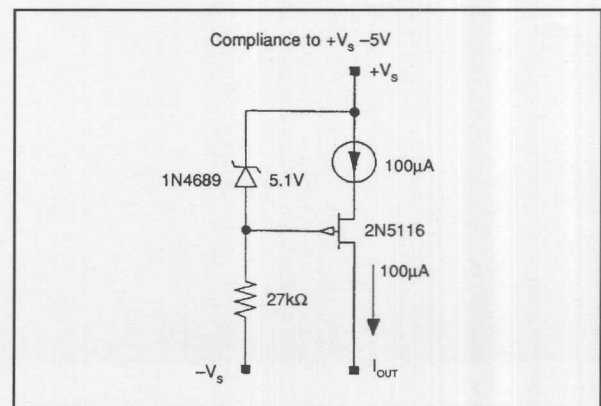



FIGURE 27. Cascoded Current Source with compliance to $-V_S + 5V$ (using zener diode for bias).

In most applications, JFETs make the best cascoding devices, but bipolar transistors and MOSFETs can also be used. MOSFETs can provide equivalent AC and DC performance to JFETs. Bipolar devices may offer better high frequency performance, but have a limited DC output impedance. The output impedance of a bipolar cascoded current source is limited by changes in base current with changes in collector voltage. The maximum output impedance of a bipolar cascoded current source is $b \cdot R_o$, where b is the current gain of the bipolar device, and R_o is its output impedance.

200 μ A Floating Cascoded Current Source Using REF200

Floating cascoded current sources with typical output impedances exceeding $10\text{G}\Omega$ can be easily implemented. Using the REF200 and a few external devices, sources of $200\mu\text{A}$, $300\mu\text{A}$, and $400\mu\text{A}$ can be strapped together.

The 200 μ A floating cascoded current source is shown in Figure 28. It is made using a cascoded current source and a cascoded current sink each biasing the other. Low voltage compliance is limited to about 8V by the sum of the gate reference voltages. High voltage compliance is limited by the lower voltage rated FET.


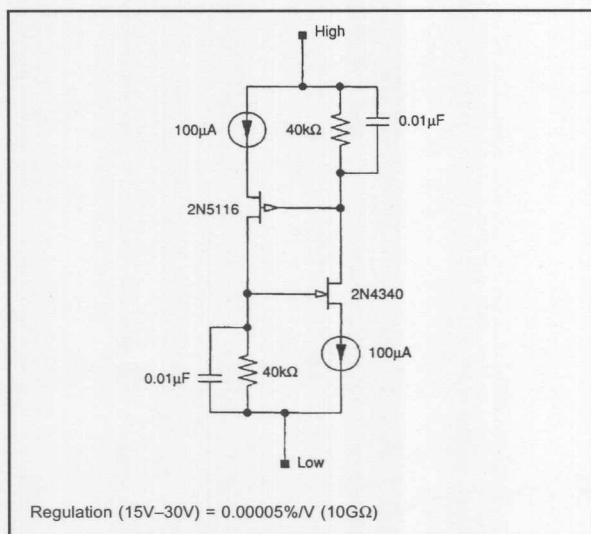
FIGURE 28. Cascoded 200 μ A Floating Current Source.

300 μ A Floating Cascoded Current Source Using REF200

The 300 μ A floating current source is shown in Figure 29. It is similar to the 200 μ A current source shown in Figure 28, except the current source in the cascoded sink section is derived from the mirror. The gate reference for the sink cascode is derived from the series combination of the mirror input and a 27k Ω resistor. The extra 100 μ A is obtained by summing the other 100 μ A current source into the sink cascode device. Compliance limits are the same as for the 200 μ A cascoded source.

400 μ A Floating Cascoded Current Source Using REF200

The 400 μ A floating cascoded current source is shown in Figure 30. It is similar to the 300 μ A cascoded current source, except that the mirror is driven by a cascoded 200 μ A current source derived by the parallel combination of the two current sources in the REF200. The low voltage compliance of this circuit is about 1V better than the previous two circuits because the mirror compliance is about 1V better. High voltage compliance is still limited only by the breakdown of the lower rated FET.

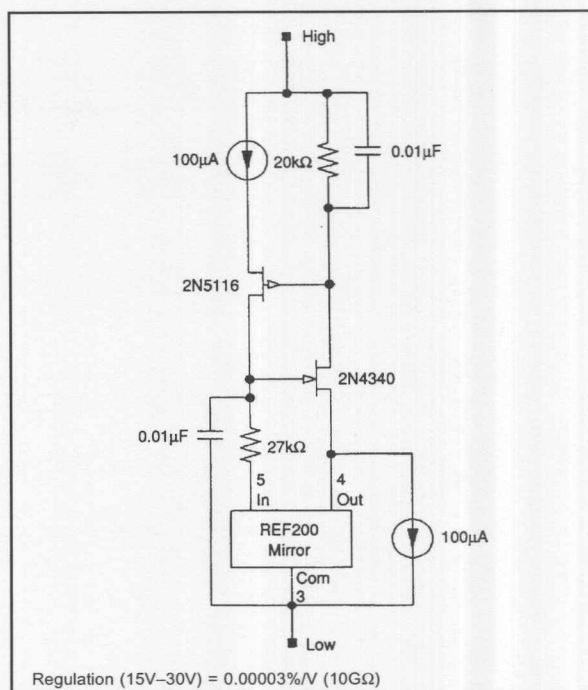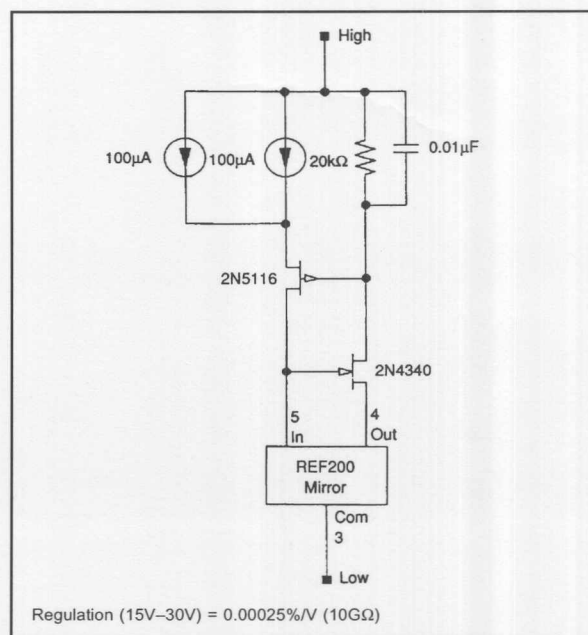FIGURE 29. Cascoded 300 μ A Floating Current Source.FIGURE 30. Cascoded 400 μ A Floating Current Source.

NOISE REDUCTION OF CURRENT SOURCES

In many modern systems, noise is the ultimate limit to accuracy. And in some systems, performance can be improved with a lower noise current source. Current source noise can be reduced by filtering, using the same basic principals used for noise reduction of voltage references. Reducing the noise bandwidth by filtering can reduce the total noise by the square root of the bandwidth reduction.

One current source noise reduction circuit is shown in Figure 31. It is basically a FET cascode circuit with the addition of an RC noise filtering circuit. The FET, as biased by the 100 μ A current source, forces an accurate DC voltage across the circuit.

Without the capacitor, noise from the current source would feed directly through to the output. The capacitor filters the noise at a -3dB frequency of $1/(2 \cdot \pi \cdot R \cdot C)$, or about 30Hz in this example. Filtering below this frequency will not reduce noise further, since the 30Hz pole is already below the 1/f corner of the current source, and noise can not be reduced by filtering in the 1/f region. Also, the noise of the FET and resistor are not filtered. Still, using this circuit, the noise is reduced from the typical 20pA/ $\sqrt{\text{Hz}}$ to less than 1pA/ $\sqrt{\text{Hz}}$.

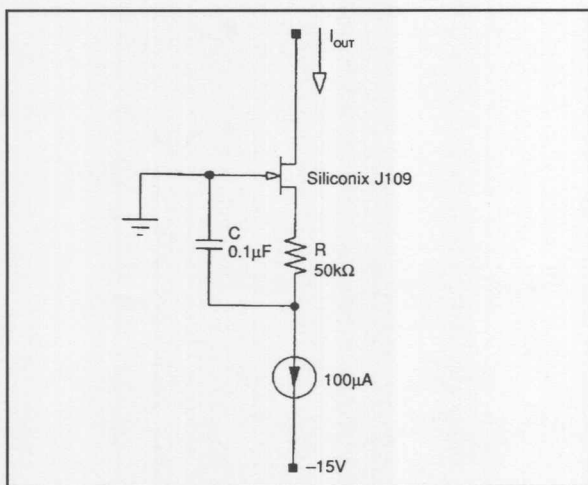


FIGURE 31. Current noise from a current source can be filtered using this circuit.

The value of the resistor used in the noise reduction circuit determines its ultimate performance. Although the noise of the resistor increases with the square root of its value, its noise degenerating effect reduces noise linearly. Therefore, the noise is reduced by the square root of the resistor increase. The practical limit for the noise reduction is the voltage drop which can be placed across the resistor.

Mathematically, current noise due to the resistor is the resistor thermal noise divided by the resistor value.

$$I_{R \text{ NOISE}} = \frac{(1.3 \cdot 10^{-10}) \sqrt{R}}{R} = (1.3 \cdot 10^{-10}) / \sqrt{R}$$

With a 50k Ω resistor, the minimum theoretical noise is .6pA/ $\sqrt{\text{Hz}}$, with 10k Ω , it is 1.3pA/ $\sqrt{\text{Hz}}$. Noise measurements of the circuit using both 10k Ω and 50k Ω resistors and the Siliconix J109 FET agree with these theoretical numbers within 20%.

The noise reduction circuit in Figure 31 has a low voltage compliance limit near ground. For compliance below ground, use the circuit shown in Figure 32.

In addition to noise reduction, these circuits have the other advantages of a FET cascoded current sink; output impedance in the G Ω region, improved AC performance, and high voltage compliance limited only by the FET.

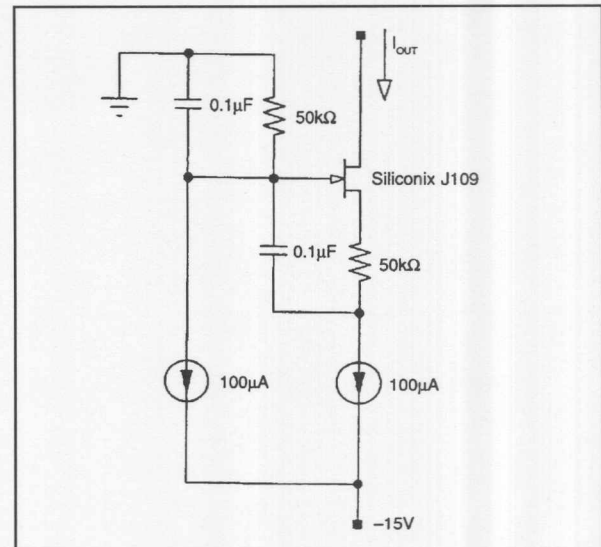


FIGURE 32. Current Noise Filtering Circuit with compliance below ground.

APPLICATIONS OF FIXED CURRENT SOURCES

VOLTAGE REFERENCES USING CURRENT SOURCES

Many design problems can be easily solved with inexpensive, easy-to-use current sources like the REF200. Although applications are endless, the collection of circuits that follows is intended to stimulate your thinking in several broad categories: fixed voltage references, floating voltage references, current excitation, fixed current references, steered current references, and biasing.

Current sources are a versatile means of forming voltage references. Why not just use a voltage reference? With a current source, a single resistor provides a programmable voltage source of any value. Low voltage references are often needed, and with this approach, it's as easy to get a 1mV reference as it is to get a 10V reference. Also, the voltage can be referenced anywhere—to the positive rail, the negative rail, or floating anywhere in between.

When impedances driven by the voltage reference are high, the voltage output from the resistor derived voltage reference can be used directly. The 100 μ V reference shown in Figure 33 can be used directly in voltage-to-frequency converter (VFC) auto-zero applications where an off-zero reference is needed (since zero frequency would take forever to measure, off-zero techniques are often used for calibrating VFCs). Where a lower output impedance is needed, a simple buffer can be added as shown in Figure 34.

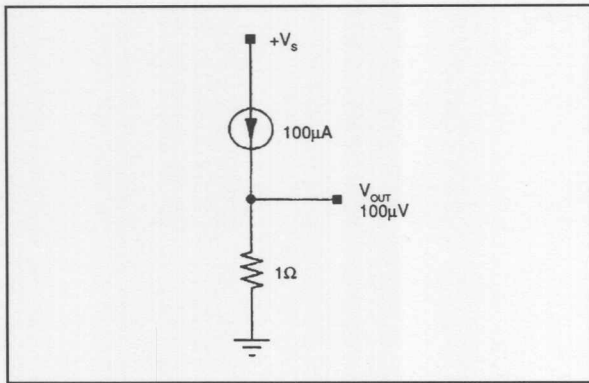


FIGURE 33. 100μV Reference for VFC off-zeroing.

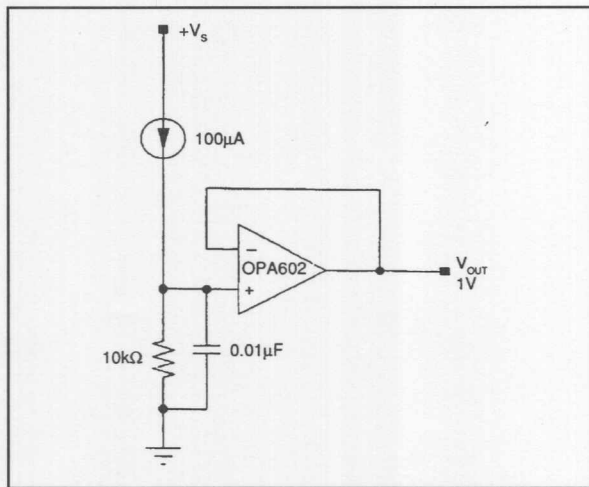


FIGURE 34. Buffered Voltage Reference.

For a floating voltage reference, simply drive the reference low side (grounded side of the voltage-setting resistor) as shown in Figure 34A. Notice that in addition to the swing limitations imposed by the op amp input common-mode range and output range, the reference high side swing is limited to 2.5V from the positive rail by the REF200's minimum compliance voltage. The low side swing is limited only by the op amp. If the reference voltage is more than about 3V this limitation can be eliminated by adding gain as shown in Figure 34B. In this example, the 1V across the reference setting-resistor is amplified to 5V at the output. Since there is always 4V between the output and the op amp inputs, the high-side swing is not limited by the current source compliance or the op amp input common mode range. It is limited only by the op amp output swing capability.

Where the voltage reference is lower than about 3V, the high side compliance will still be limited by the current source compliance. In these situations, consider the circuit shown in Figure 34C. In this case, the op amp noninverting input is driven while the current source connects to the other op amp input and a voltage setting resistor with its other terminal

connected to the output. High-side compliance is limited only by the op amp. Another advantage of this circuit is its high input impedance. The disadvantage is limited low side compliance. Current source compliance limits swing to the negative rail to 2.5V — regardless of the op amp input common mode range.

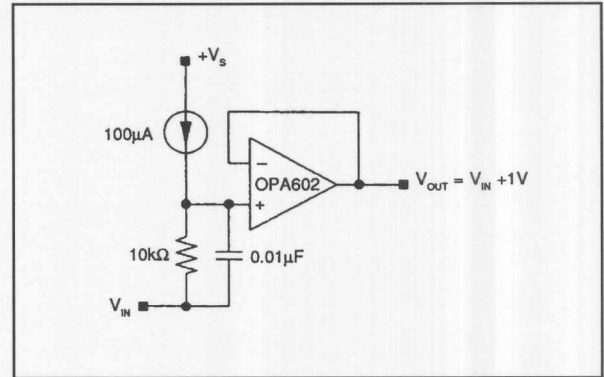


FIGURE 34A. Floating Voltage Reference.

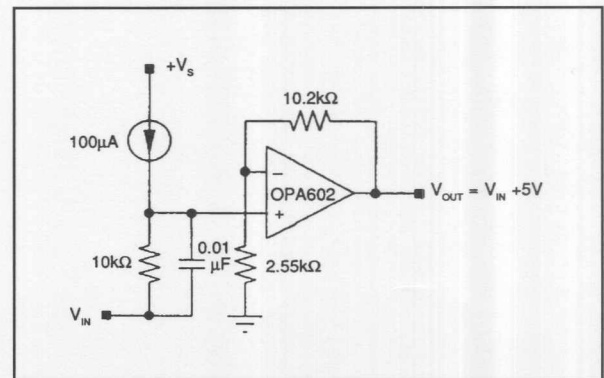


FIGURE 34B. Floating Voltage Reference with high-side compliance limited only by op amp output swing capability.

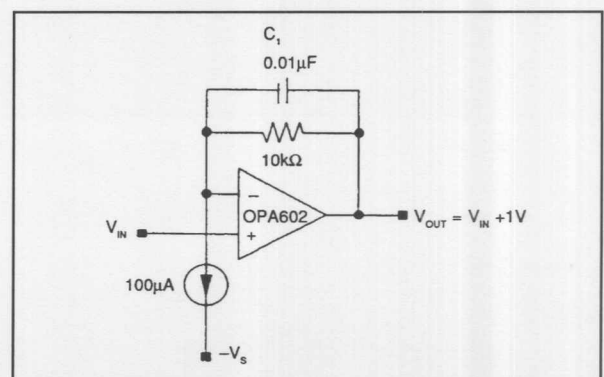


FIGURE 34C. Floating Low Voltage Reference with high impedance input drive and high-side output compliance limited only by op amp output swing capability.

OP AMP OFFSET ADJUSTMENT USING 5mV REFERENCE

Op amp offset adjustment circuits are another application for millivolt level references. Many op amps, especially duals and quads, have no built-in provision for offset adjustment. Even when offset adjustment pins are provided, using them can degrade offset voltage drift and stability (e.g. the drift of a typical bipolar input op amp is increased $3\mu\text{V}/^\circ\text{C}$ for each millivolt of offset adjustment). External offset adjustment circuits are commonly used to solve these problems.

Conventional external offset adjustment circuits can add problems of their own. Many of these circuits use the op amp power supplies as references. Power supply variation feeds directly into the op amp input. This error appears as poor power supply rejection. Likewise, noise from the power supplies appears as op amp input referred noise.

The circuits shown in Figures 35 and 36 solve these problems. REF200 current sources provide regulated $\pm 5\text{mV}$ references for stable offset adjustment. This approach provides a truly precision offset adjustment free from problems associated with power supply variations, noise, and drift.

The circuit shown in Figure 35 uses a pair of 51Ω resistors connected to ground to establish the $\pm 5\text{mV}$ reference. A pot connected across this reference allows a $\pm 5\text{mV}$ offset adjustment range. Additional pots can be connected, but be sure to maintain a parallel resistance $>50\Omega$ to get $>\pm 5\text{mV}$ range.

The second circuit, Figure 36, uses a special potentiometer manufactured by Bourns. It is especially designed for op amp offset adjustment. It has a tap at the center of the element which can be connected to ground. Using this connection eliminates the 51Ω resistors needed in the first circuit.

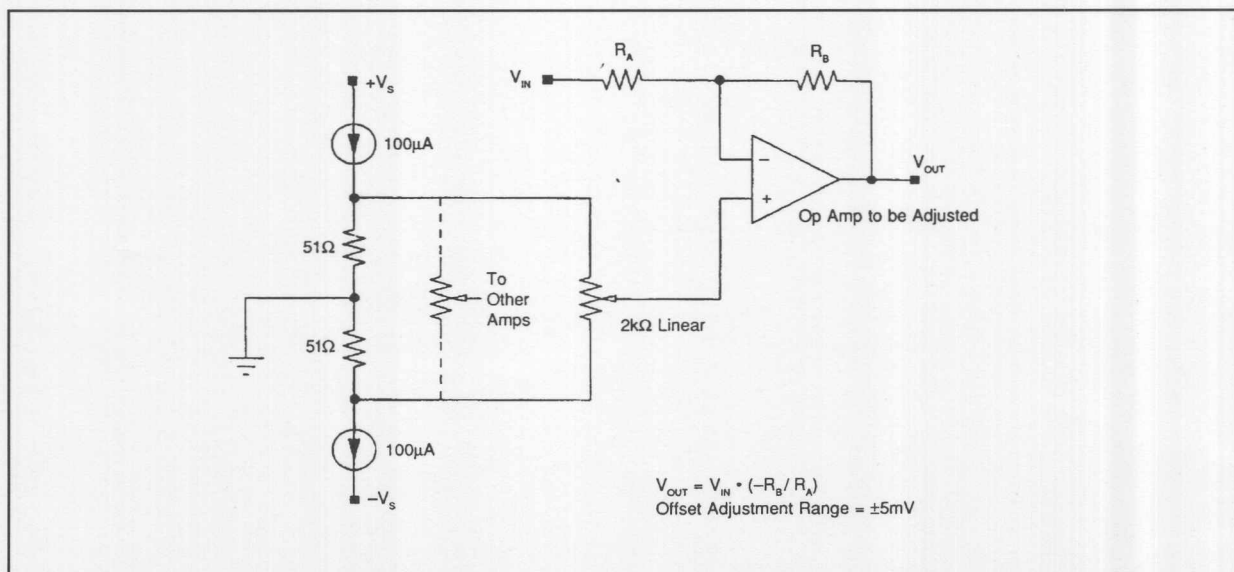


FIGURE 35. Op Amp Offset Adjustment Circuit uses the two $100\mu\text{A}$ current sources from a REF200 to provide accurate $\pm 5\text{mV}$ references.

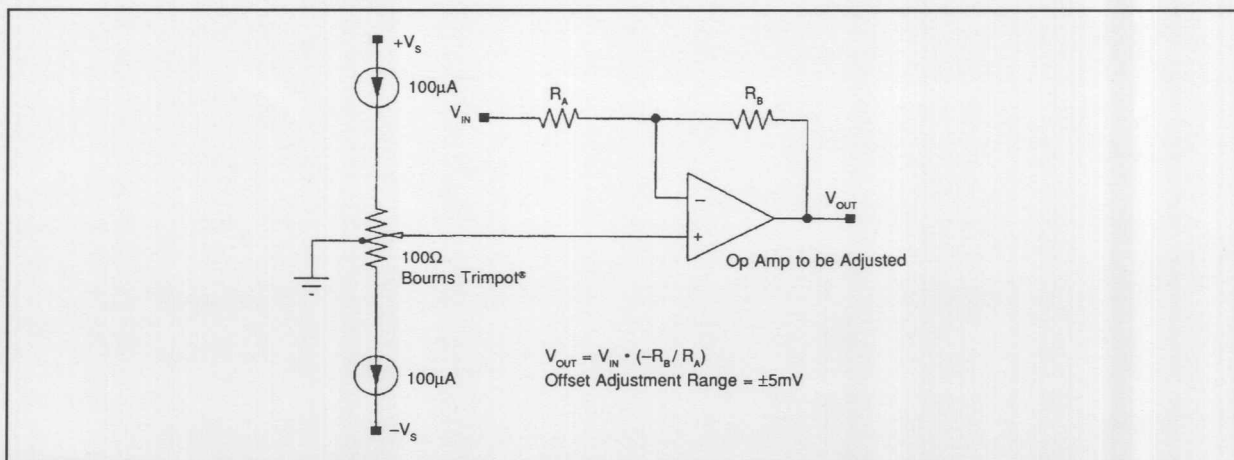


FIGURE 36. Op amp offset adjustment circuit using Bourns Trimpot®.

WINDOW COMPARATOR USING FLOATING VOLTAGE REFERENCE

The window comparator circuit, Figure 37, is an example of a floating reference application. Here, a pair of current sources driven by the V_{CENTER} input. V_O is low when V_I is either above $V_{\text{CENTER}} + 100\mu\text{A} \cdot R$, or below $V_{\text{CENTER}} - 100\mu\text{A} \cdot R$. Otherwise, V_O is high. By using different values for the programming resistors, the threshold can be set asymmetrically around V_{CENTER} if desired.

RTD EXCITATION USING CURRENT REFERENCE

Current sources are often used for excitation of resistor type sensors such as RTDs. If the RTD is located remotely, as it often is, voltage drops in the interconnecting wire can cause

excessive errors. The usual solution to this problem is to use four wire Kelvin connections. Two wires are used to carry the current excitation signal to the RTD. The other two wires sense the voltage across the RTD. With no current flowing in the sense connection, there is no error due to wire resistance.

One problem is that the additional wiring can be very expensive. The three wire circuit shown in Figure 38 saves one wire. $200\mu\text{A}$ is used for excitation of a $1\text{k}\Omega$ RTD, and a matching current from the current mirror is forced in the ground connection. The voltage drops through the two wires cancel thereby eliminating error.

Notice also, that one common wire (shown as a shield) can serve multiple sensors. Each additional RTD only needs one additional pair of wires.

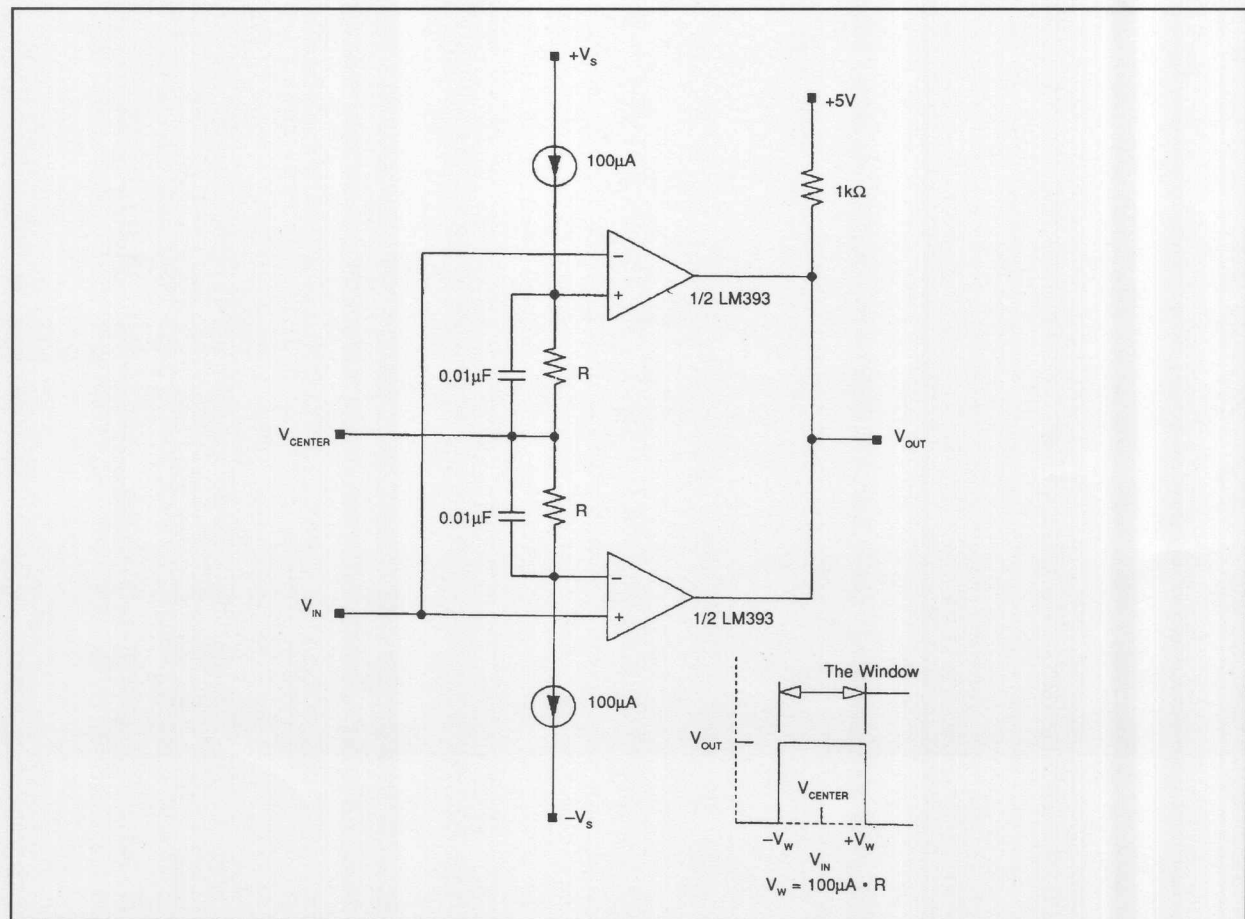


FIGURE 37. Window comparator with voltage programmable window center, and resistor programmable window width.

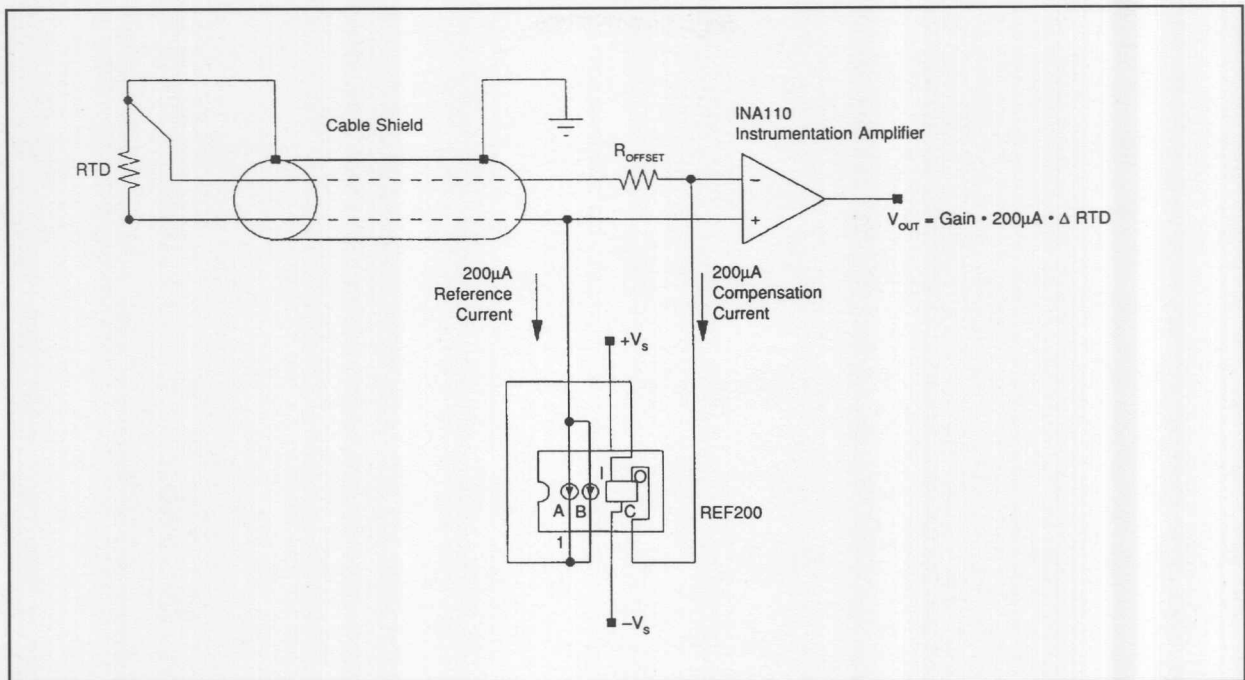


FIGURE 38. RTD excitation with three-wire lead resistance compensation.

DEAD BAND CIRCUITS USING CURRENT REFERENCE

Servo control systems frequently use dead-band and limiting circuits. The precision dead-band circuit shown in Figures 39 and 40 demonstrates the use of a current source as a fixed reference. To understand how it works, notice that, without the current reference, the circuit is an inverting half wave rectifier. Positive inputs drive the op amp output negative and feedback is through forward biased D_1 . No current flows through reverse biased D_2 , and the output is held at virtual ground by R_2 .

Negative inputs forward bias D_2 and drive the output positive. Feedback to the output through R_2 eliminates error due to the diode drop, and the circuit functions as a precision

unity gain inverter ($V_o = -V_i$). (Adding the current reference pre-biases to the input so that the output remains at virtual ground until the input current through R_1 exceeds $100\mu A$.) The output is zero (dead) until $V_i < \pm 100\mu A \cdot R_1$. An alternate approach would be to pre-bias the input through a precision resistor connected to a voltage reference, but that would add noise gain increasing offset, drift, and noise at the output.

For a negative dead-band use the circuit shown in Figure 40. It's the same circuit with the diodes reversed.

For a double dead-band, use the circuit shown in Figure 41. It uses both the positive and negative dead-band circuits summed together by a third amplifier.

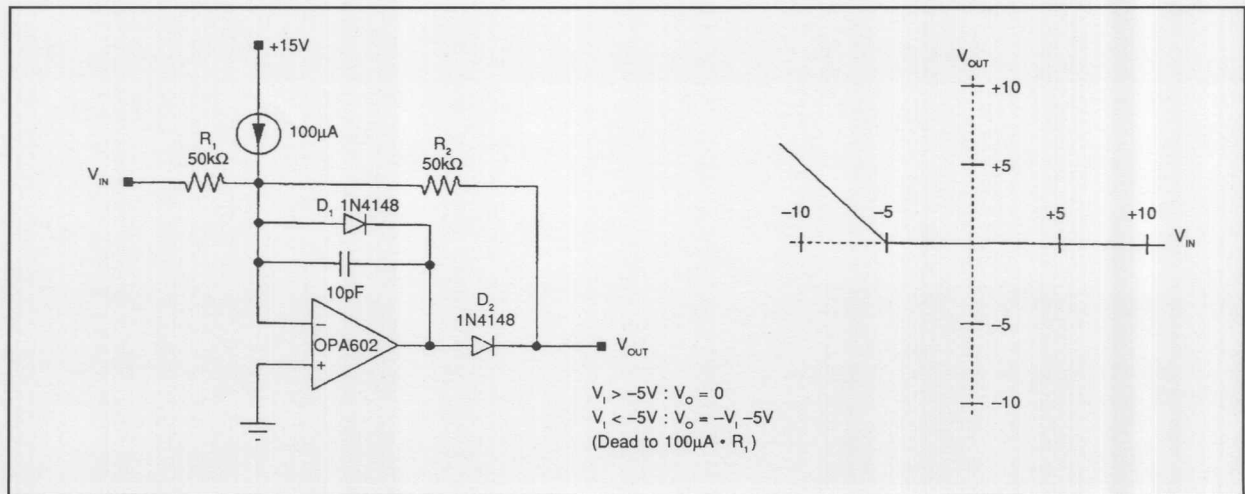


FIGURE 39. Precision positive dead-band circuit.

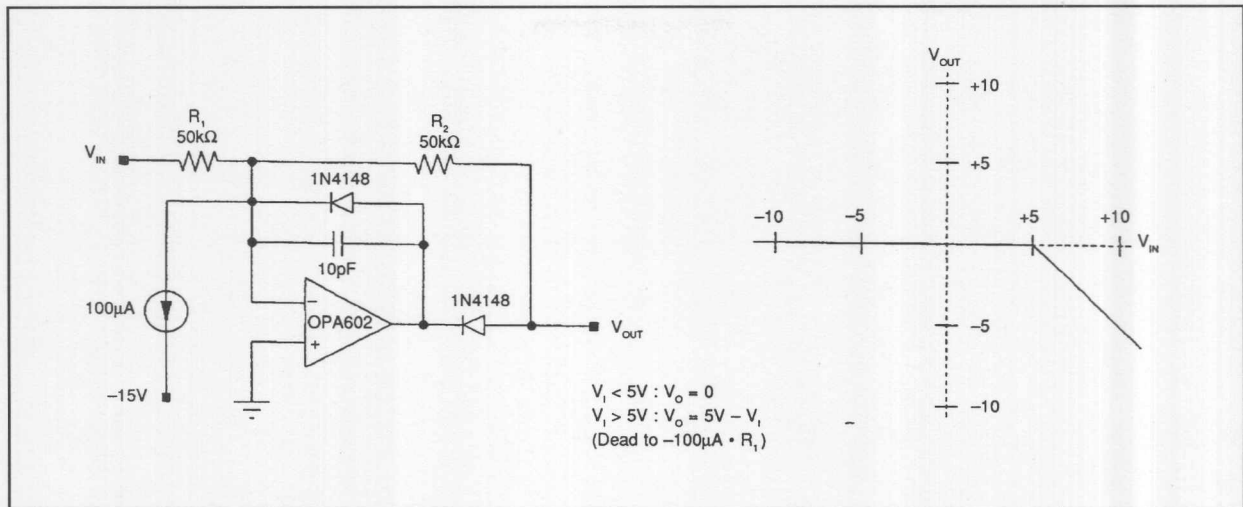


FIGURE 40. Precision negative dead-band circuit.

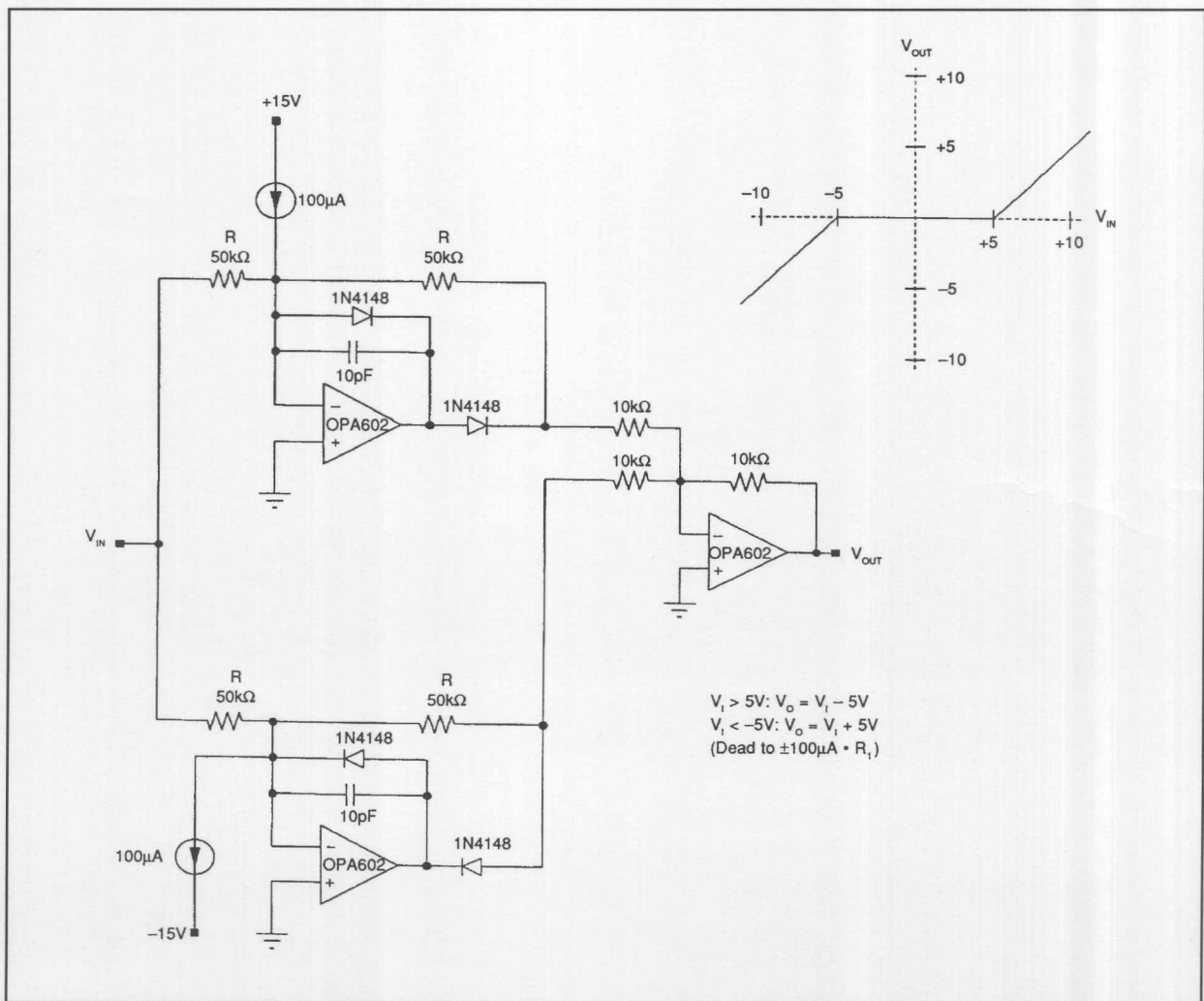


FIGURE 41. Precision double dead-band circuit.

BIDIRECTIONAL CURRENT SOURCES

One of the advantages in working with currents is that they can be steered by diodes or switches without error. As long as no current is lost through leakage, voltage drops in series with current signals do not diminish their accuracy.

The bidirectional current source shown in Figure 42 is a versatile circuit building block and an excellent example of diode steering. This two-terminal element is basically a full-wave bridge rectifier circuit with a current source connected between its DC terminals. A positive signal on the left terminal with respect to the right reverse biases D_3 and D_4 and accurately steers current through D_1 and D_2 . A negative signal reverses the situation and accurately steers the same current in the opposite direction.

For one diode drop better compliance, use the bidirectional current source shown in Figure 43. The disadvantages of this circuit are that two current sources are required, and the inherent current matching of the previous circuit is lost.

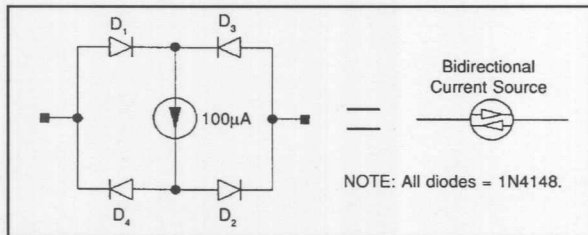


FIGURE 42. Bidirectional current source.

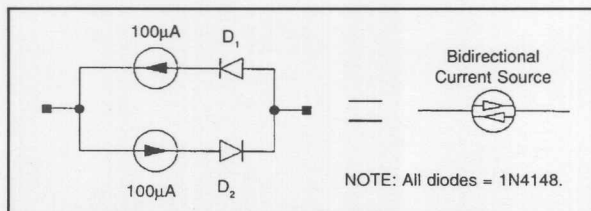


FIGURE 43. Bidirectional current source with improved compliance.

LIMITING CIRCUITS USING BIDIRECTIONAL CURRENT SOURCES

The precision double limiting circuit shown in Figure 44 puts the bidirectional current source to work. To understand how this circuit works, notice that without R_1 , it functions as a precision unity-gain amplifier. The input signal is connected to the non-inverting terminal of A_1 . Feedback to the inverting terminal is through the bidirectional current source, voltage-follower connected A_2 , and the $1k\Omega$ resistor. When less than $100\mu A$ is demanded from the current source, it saturates and the total voltage drop across the bidirectional current source is less than about 2V plus two diode drops. Since no current flows in the $1k\Omega$ resistor, the circuit output voltage must equal the input voltage and errors due to A_2 and the drop across the current source are eliminated. The $1k-100pF$ network provides compensation for the extra phase shift in the feedback loop.

When R_1 is added, the circuit still functions as a follower for small signals where the current through R_1 is less than $100\mu A$. When the current reaches $100\mu A$, the current source becomes active and limits the output voltage. With the bidirectional current source, the circuit limits symmetrically in both directions.

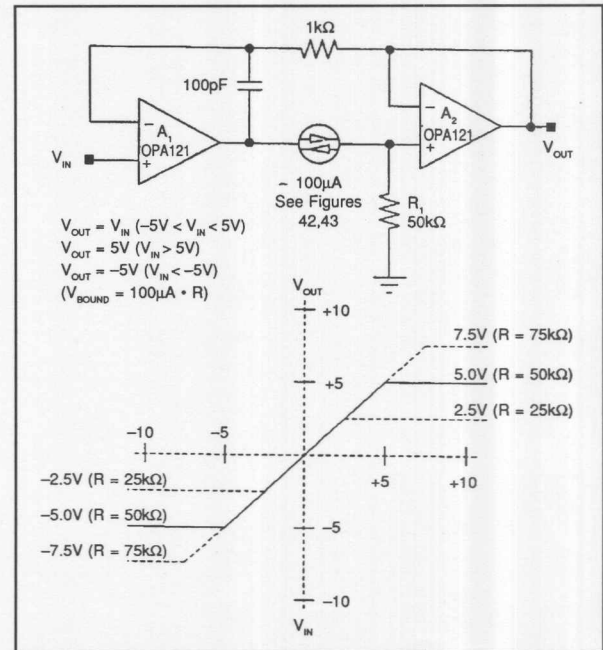


FIGURE 44. Precision double limiting circuit.

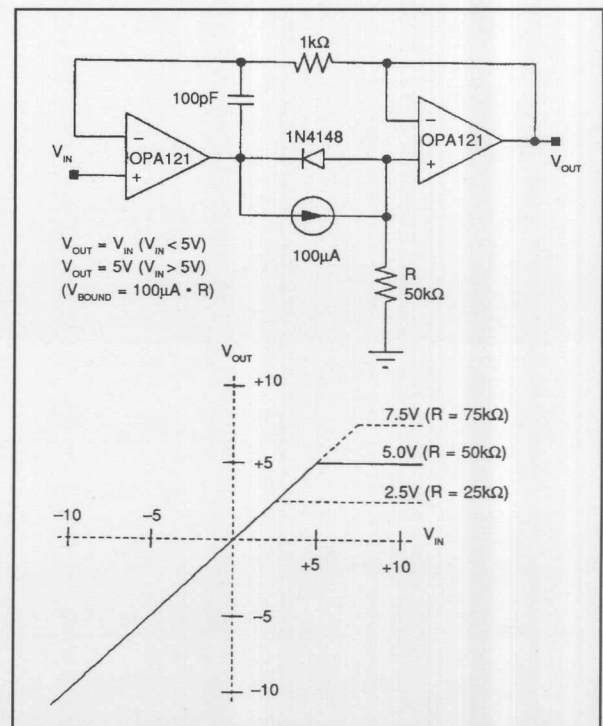


FIGURE 45. Precision limiting circuit.

If a limit in just one direction is required, replace the bidirectional current source with a current source and single diode as shown in Figure 45. For limiting in the opposite direction, reverse the polarity of the current source and diode.

PRECISION TRIANGLE WAVEFORM GENERATOR USING BIDIRECTIONAL CURRENT SOURCES

The precision triangle waveform generator shown in Figure 46 makes use of two bidirectional current sources. One steers a precision current signal into the integrating capacitor connected to the inverting input of the op amp. The other steers a precision current into the $10k\Omega$ resistor connected to the positive op amp terminal to provide $\pm 1V$ hysteresis. The result is a relaxation oscillator with precision triangle and square wave outputs of $\pm 1V$.

DUTY CYCLE MODULATOR USING BIDIRECTIONAL CURRENT SOURCES

The precision duty cycle modulator shown in Figure 47 is a variation of the triangle generator. Here the integrating capacitor is replaced by a true integrator formed by A_1 and C . This allows the summation of a ground referenced signal through the $100k\Omega$ input resistor. With no input signal, the output is a square wave with 50% duty cycle. Input signals sum into the integrator through the $100k\Omega$ resistor. The integrator then slews faster in one direction, and slower in the other. The result is a linear duty cycle modulation of the output signal. The modulator is said to be duty cycle rather than pulse width because the output frequency varies somewhat with input signal. For a constant frequency duty cycle modulator add a resistor in series with the inverting input of A_2 and drive that input with a resistor coupled clock signal.

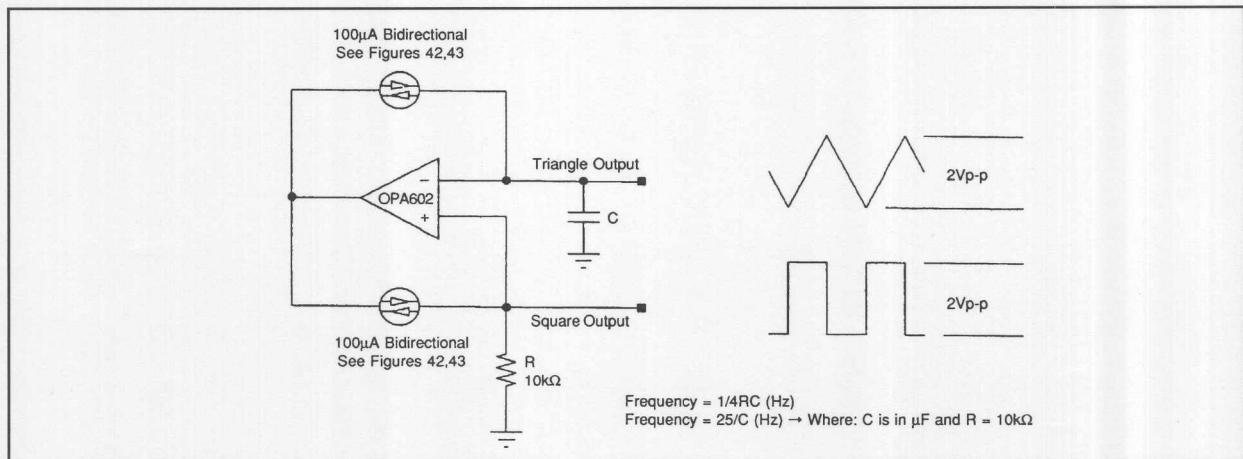


FIGURE 46. Precision triangle waveform generator.

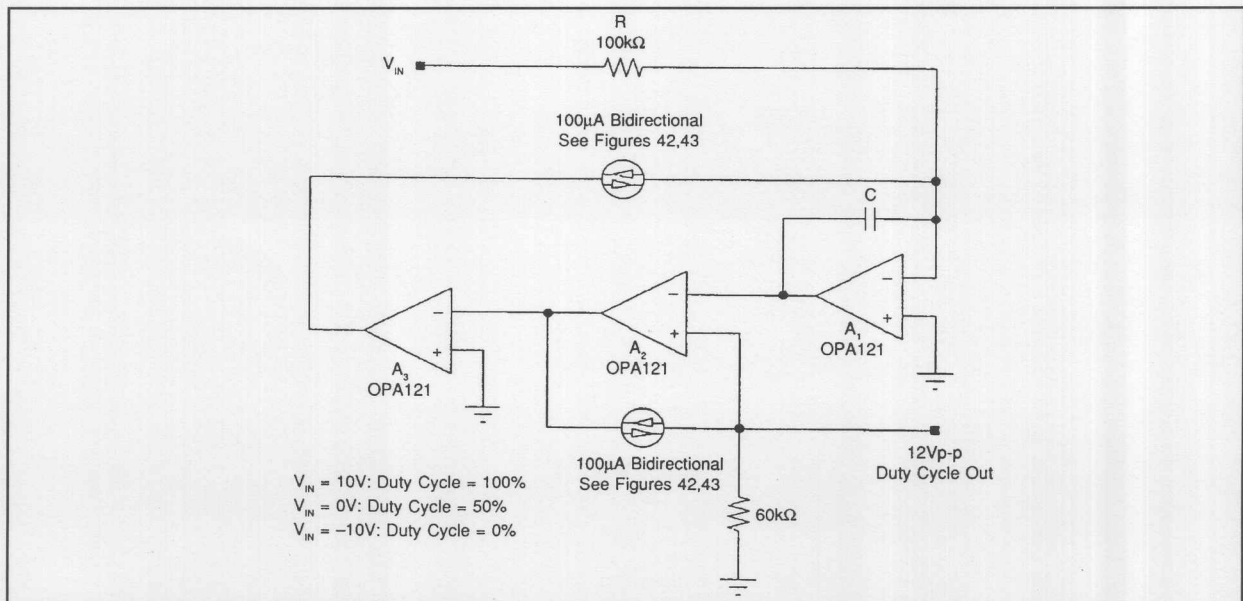


FIGURE 47. Precision duty-cycle modulation circuit.

Notice that the duty-cycle modulator has a true integrating input. This is in contrast to conventional modulators which simply use a comparator connected between the input signal and a precision triangle wave. With the conventional approach, at crossing, input noise feeds through at the comparator bandwidth resulting in jitter. Not only does the integrating input filter out input noise, it can be synchronized to input noise (such as 60Hz), completely notching out its effect. If integration takes place over one or more complete cycles of the noise signal, the undulations of the noise signal are exactly averaged out.

SLEW RATE LIMITER

In some applications, especially when driving inductors, it is necessary to limit the signal slew rate. The rate limiting circuit shown in Figure 48 uses a diode bridge for current steering in a different way. Here two current sources are connected, one to the positive terminal and one to the negative terminal, of the bridge. Without the capacitor, the circuit would act as a unity gain inverting amplifier. Feedback through the $10\text{k}\Omega - 10\text{k}\Omega$ resistor network drives the left side of the bridge. The right side of the bridge follows, driving the op amp inverting input. Voltage offset due to diode mismatch can be mitigated by using a monolithic bridge such as the one specified. When the integrator capacitor is added, charging and discharging current must flow to maintain the virtual ground. But when that current exceeds $100\mu\text{A}$, the bridge reverse biases limiting the output slew rate to $100\mu\text{A}/^\circ\text{C}$ regardless of input signal rate.

SINGLE SUPPLY INSTRUMENTATION AMPLIFIER

Single power supply systems are common and the need for instrumentation amplifiers (IAs) to operate in this environ-

ment is critical. While single supply op amps have been available for many years, single supply IAs have not. What's more, single supply IAs can not be made by simply using single supply op amps in the traditional manner. In a conventional IA topology the outputs as well as the inputs would need to swing to the negative rail. Although some op amps come close, no amplifier output can swing all the way to its power supply rail, especially when driving a load.

The single supply IA circuit shown in Figure 49 solves this problem by simply level shifting the input signal up by a V_{be} with a matched pair of matched PNP input transistors. The transistors are biased as emitter followers by the $100\mu\text{A}$ current sources in a REF200. The ensuing circuit is a traditional three op amp IA. OPA1013s are used for input amplifiers because they are designed for single supply operation and their output can also swing near the negative rail. The Burr-Brown INA105 is used as a difference amplifier. All critical resistor matching is taken care of by the INA105. The common mode range of the single supply IA typically extends to 0.5V below the negative rail with a typical CMR better than 86dB .

VOLTAGE CONTROLLED CURRENT SOURCE USING INA105

The modified Howland current pump (Figures 50-52) is an extremely versatile voltage controlled current source. Since it has differential inputs, you can ground one input and drive the other to get either an inverting or noninverting transfer function. If you drive both inputs, the output current will be proportional to the voltage difference between the inputs.

What's more, unlike current sources made with a series pass element, which can either sink or source current, this current source has a bipolar output. It can both sink and source current.

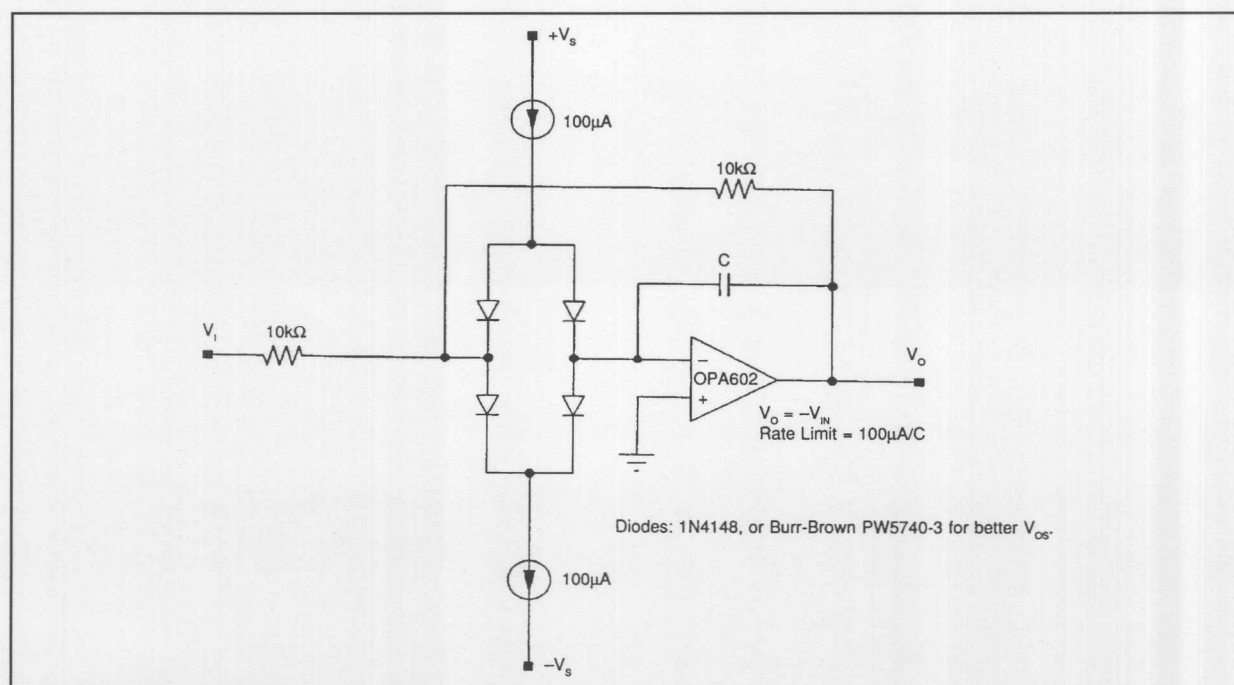


FIGURE 48. Rate limiting circuit.

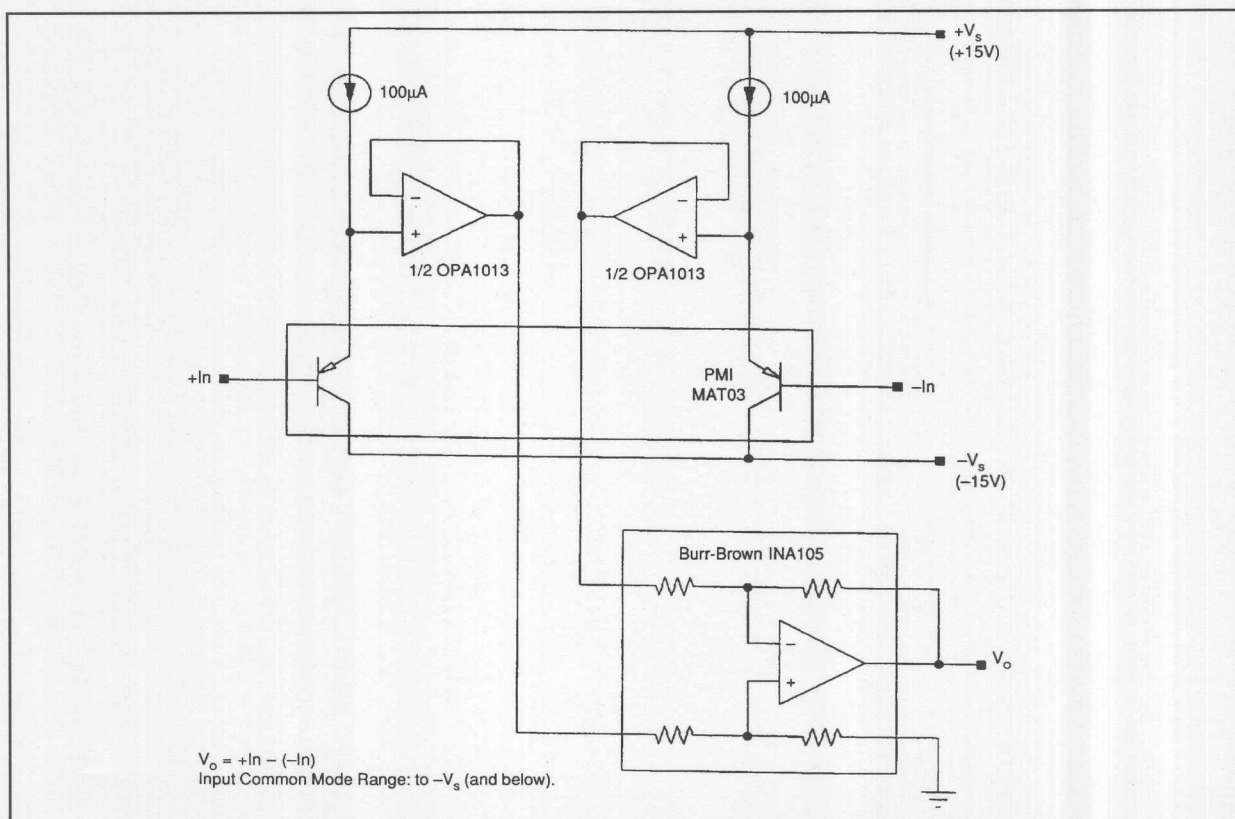


FIGURE 49. Single-supply instrumentation amplifier.

Use of this circuit was limited in the past due to the critical resistor matching and resistor TCR tracking requirements. By using the INA105 difference amplifier, the circuit can be easily implemented with the addition of two 1% resistors. Matching of the external resistors is important, but since they add to the internal 25kΩ resistors, the matching requirement is divided down by the ratio of resistance.

Output impedance of the current source is proportional to the common mode rejection (CMR) of the difference amplifier. Mismatch of feedback resistors in the difference amplifier.

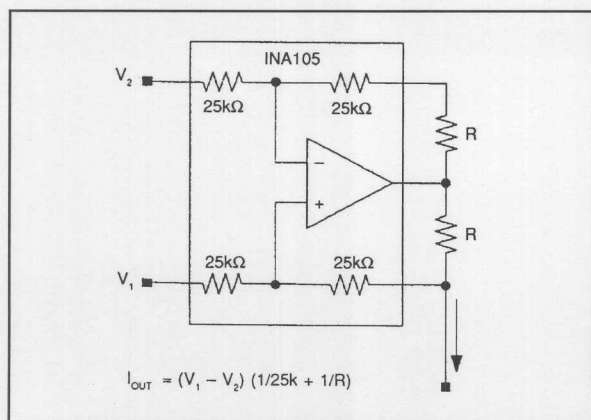


FIGURE 50. Voltage-controlled current source with differential inputs and bipolar output.

fier caused by the external resistors will degrade CMR and lower the current source output impedance. Resistor match of 0.002% is required for 100dB CMR in a unity gain difference amplifier. Depending on the value of the external resistor and output impedance requirement, it may be necessary to trim the external resistor.

When the value of the external resistor becomes large consider the alternate circuit shown in Figure. 51.

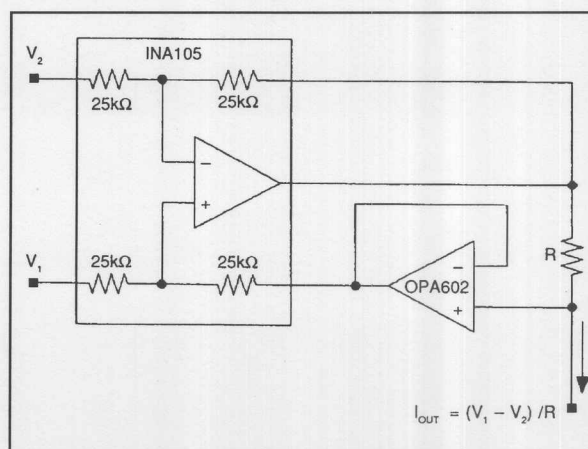


FIGURE 51. Voltage-controlled current source with differential inputs and bipolar output and circuit to eliminate feedback resistor error.

You need an extra amplifier to drive the feedback resistor in the difference amplifier, but only one external resistor is required, and no matching or trimming is needed.

In any case the output impedance of the current source can be approximated by the following relationship:

$$Z_o = R_x \cdot 10^{[CMRR/20]}$$

Where:

Z_o = equivalent output impedance of current source [Ω]

CMRR = difference amp common mode rejection ratio [dB]

(for Figure 50)

R_x = parallel combination of external resistor and 25k Ω

$$R_x = \frac{R \cdot 25k\Omega}{R + 25k\Omega}$$

(for Figure 51)

R_x = external resistor [Ω]

The INA105 can source 20mA and sink 5mA. If higher output current is required, add a current buffer as shown in Figure 52. The OPA633 shown allows output currents up to ± 100 mA. Since the buffer is within the feedback loop, its DC errors have no effect on the accuracy of the current source. When using other buffers make sure that their bandwidth is large enough not to degrade circuit stability.

If you want voltage gain in the voltage to current converter, use the INA106 for a gain-of-ten difference amplifier.

Don't forget that source impedance adds directly to the input resistors of the difference amplifier which can degrade its performance. A source impedance mismatch of 5 Ω will degrade the CMRR of the INA105 to 80dB. If you are driving the circuit from an amplifier or other low impedance source, this should not be a problem. If you have higher source impedances, buffer the driven input(s) of the difference amplifier, or use an instrumentation amplifier such as the INA110 instead of a difference amplifier.

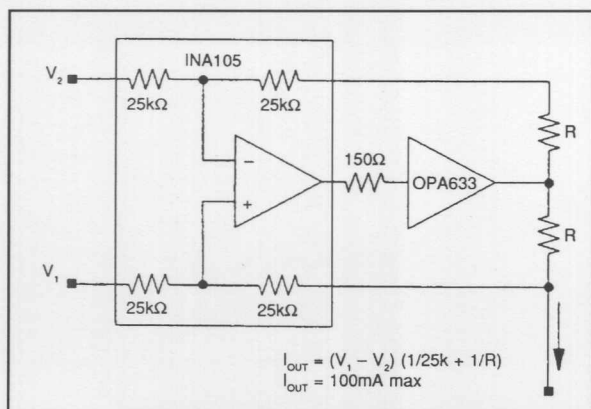


FIGURE 52. Voltage-controlled current source with differential inputs and current boosted bipolar output.

VOLTAGE CONTROLLED CURRENT SOURCE WITH INSTRUMENTATION AMPLIFIER INPUT—THE XTR101

The XTR101 is a floating current source designed for two wire 4-20mA current loop applications. It is a voltage controlled current source with a precision instrumentation amplifier input. It also contains two matched 1mA current sources which makes it suited for remote signal conditioning of a variety of transducers such as thermocouples, RTDs thermistors, and strain gauge bridges.

Figure 53 shows the XTR101 connected as a temperature controlled current source. The temperature sensing element is a thermocouple, and cold junction compensation is provided by the diode.

The product data sheet for the XTR101, (PDS-627) gives operating details for the device and shows several other applications.

SINGLE SUPPLY VOLTAGE CONTROLLED CURRENT SOURCE—THE XTR110

The XTR110 is a precision single supply voltage to current converter. Although it is designed specifically for three wire 4-20mA current transmission it can also be used in more general voltage to current source applications. As shown in Figure 54, it contains: a precision 10.0V reference and input resistor network for span offsetting (0V In = 4mA Out), a voltage to current converter for converting a ground referenced input signal to an output current sink, and a current mirror for turning the output of the current sink into a current source.

The current mirror has a gain ratio of 10:1 and uses an external pass transistor to minimize internal thermal feedback and improve accuracy. Since the mirror transistor is external, an external mirror ratio setting resistor can be added for an arbitrarily high output current.

Both the voltage to current converter, and the current mirror use single supply op amps so that the input and output signals can go to zero. In the case of the mirror op amp, the common mode range goes to the positive power supply rail rather than common.

The following table shows a range of input-output spans that is available simply by pin strapping the XTR110.

Input Range (V)	Output Range (mA)	Pin 3	Pin 4	Pin 5	Pin 9	Pin 10
0-10	0-20	Com	Input	Com	Com	Com
2-10	4-20	Com	Input	Com	Com	Com
0-10	4-20	+10	Input	Com	Com	Open
0-10	5-25	+10	Input	Com	Com	Com
0-5	0-20	Com	Com	Input	Com	Com
1-5	4-20	Com	Com	Input	Com	Com
0-5	4-20	+10	Com	Input	Com	Open
0-5	5-25	+10	Com	Input	Com	Com

For more details and applications, request product data sheet PDS-555.

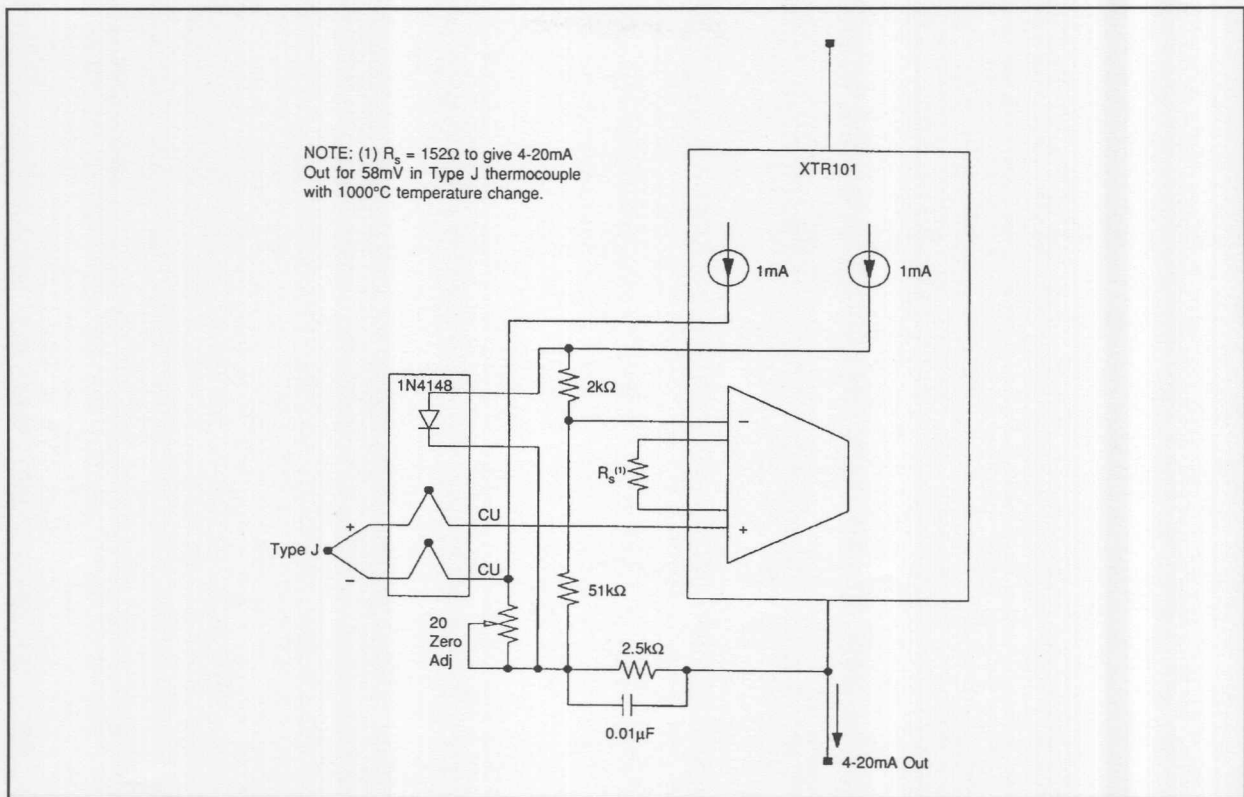


FIGURE 53. Temperature-controlled current source using XTR101.

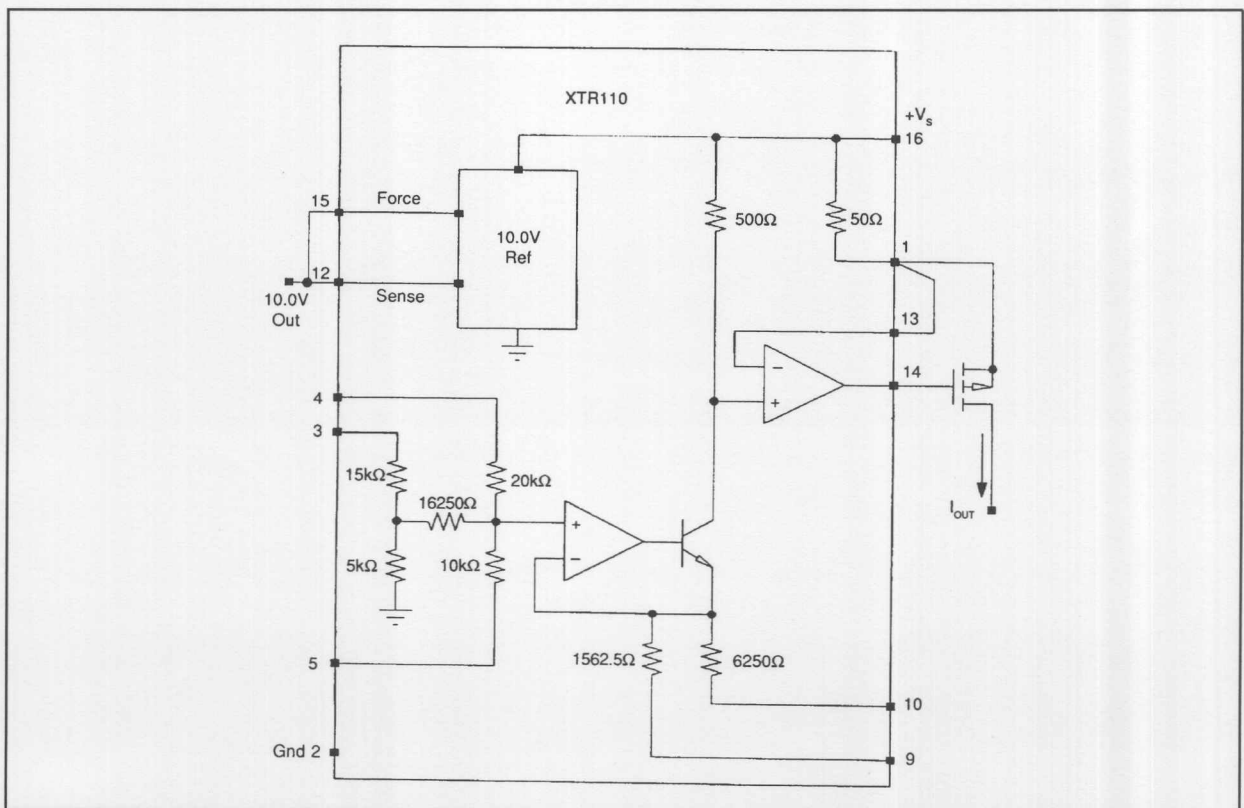


FIGURE 54. Precision single-supply voltage-to-current source transmitter—the XTR110.

CURRENT RECEIVER WITH COMPLIANCE TO BOTH POWER SUPPLY RAILS USING THE INA105

Measuring current signals can be as simple as feeding the current into a precision resistor ($V = I \cdot R$). If needed, the voltage developed across the resistor can be buffered or amplified with an operational amplifier.

If common-mode signals are present on the current return end of the sense resistor, an instrumentation amplifier (IA) can be used to reject the common mode signal and reference the output signal to ground. However, a limitation of conventional IAs is that their common mode input range is limited to less than 10V.

When you need to reference the current return of the sense resistor to a higher common mode voltage, consider one of the following difference amplifiers.

Model	Input Common Mode Range	Other Features
INA105	(1) $\pm 20V$	(2)
INA117	$\pm 200V$	
RCV420	$\pm 40V$	

NOTES: (1) Common-mode input range specified for operation on standard $\pm 15V$ power supplies. (2) Also contains a precision reference and offsetting circuitry to get 0-5V outputs with 4-20mA inputs.

Figure 55 shows a current receiver using the INA105. The input current signal is sensed across 100Ω resistor, R_s , connected to the negative power supply rail. Connecting the sense resistor to a power supply rail instead of ground maximizes the voltage drop available across the current transmitter.

Voltage divider action of the feedback resistors within the INA105 divide the common-mode input by two. Therefore, common mode input signals of up to $\pm 20V$ are attenuated to an acceptable level of no more than $\pm 10V$ at the op amp inputs.

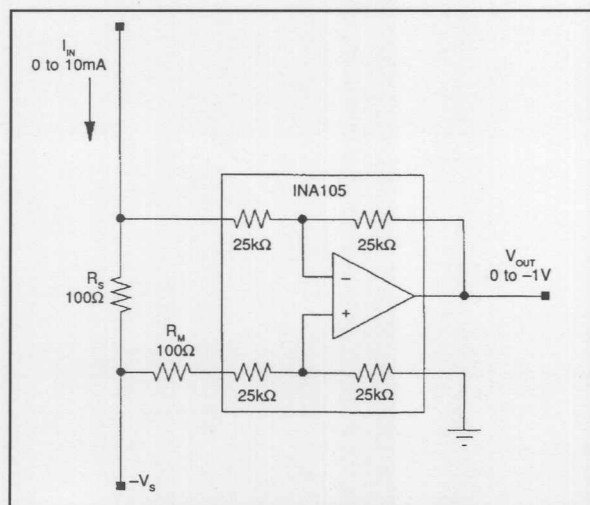


FIGURE 55. Current-to-voltage converter referenced to the negative power supply rail.

Matching resistor, R_M , preserves the resistance match of the INA105 and maintains its high common-mode rejection (CMR). Because 100Ω is small compared to the $25k\Omega$ difference resistors, a 1% tolerance is sufficient to maintain 86dB CMR.

The INA105 references the output signal to ground with a gain of one. For a 0-10mA input the output is 0 to -1V (a transfer function of -100V/A). If a positive transfer function is desired, interchange the input pins of the difference amplifier. To reference current signals to the positive rail, simply connect the sense resistor and the other difference amplifier input to that point.

The $25k\Omega$ input impedance of the difference amplifier causes a slight error by shunting a portion of the input current signal. In the noninverting configuration, the matching resistor lowers the difference amplifier gain, but since the shunting input impedance of the noninverting input is $50k\Omega$, for a unity gain difference amp, the error turns out to be the same. For a 100Ω sense resistor, the error is approximately 0.4%. For better accuracy, select a slightly higher value sense resistor to compensate for the error according to the following equation.

$$R_s = R_M = \frac{25k \cdot X}{25k - X}$$

Where:

X = desired transfer function [V/A]

For example:

For 1V/10mA (100V/A) from Figure 55:

$$R_s = R_M = 100.4\Omega$$

POWER AMP LOAD CURRENT MONITORING USING THE INA105 OR THE INA117

The INA117 is a difference amplifier similar to the INA105 except that it has a 20/1 input divider allowing a $\pm 200V$ common mode input range. It also has an internal gain of 20 providing an overall gain of one. The penalty is that amplifier DC errors, and resistor and amplifier noise are amplified by 20. Still for 200V applications that do not require galvanic isolation its has better performance than isolation amplifiers, and it does not require an isolated power supply.

Figure 56 shows a circuit for measuring load current in a bridge amplifier application using the INA117. At low frequencies, a sense resistor could be inserted in series with the load, and an instrumentation amplifier used to directly monitor the load current. However, under high frequency or transient conditions, CMR errors would limit accuracy. This approach eliminates these problems by gleaning the load current from measurements of amplifier supply current.

The power supply current of one of the bridge op amps is measured using INA117s and 0.2Ω sense resistors connected to the power supplies. Because the 0.2Ω sense resistor adds negligible resistance error to the $380k\Omega$ input resistors of the INA117s, no matching resistors are required.

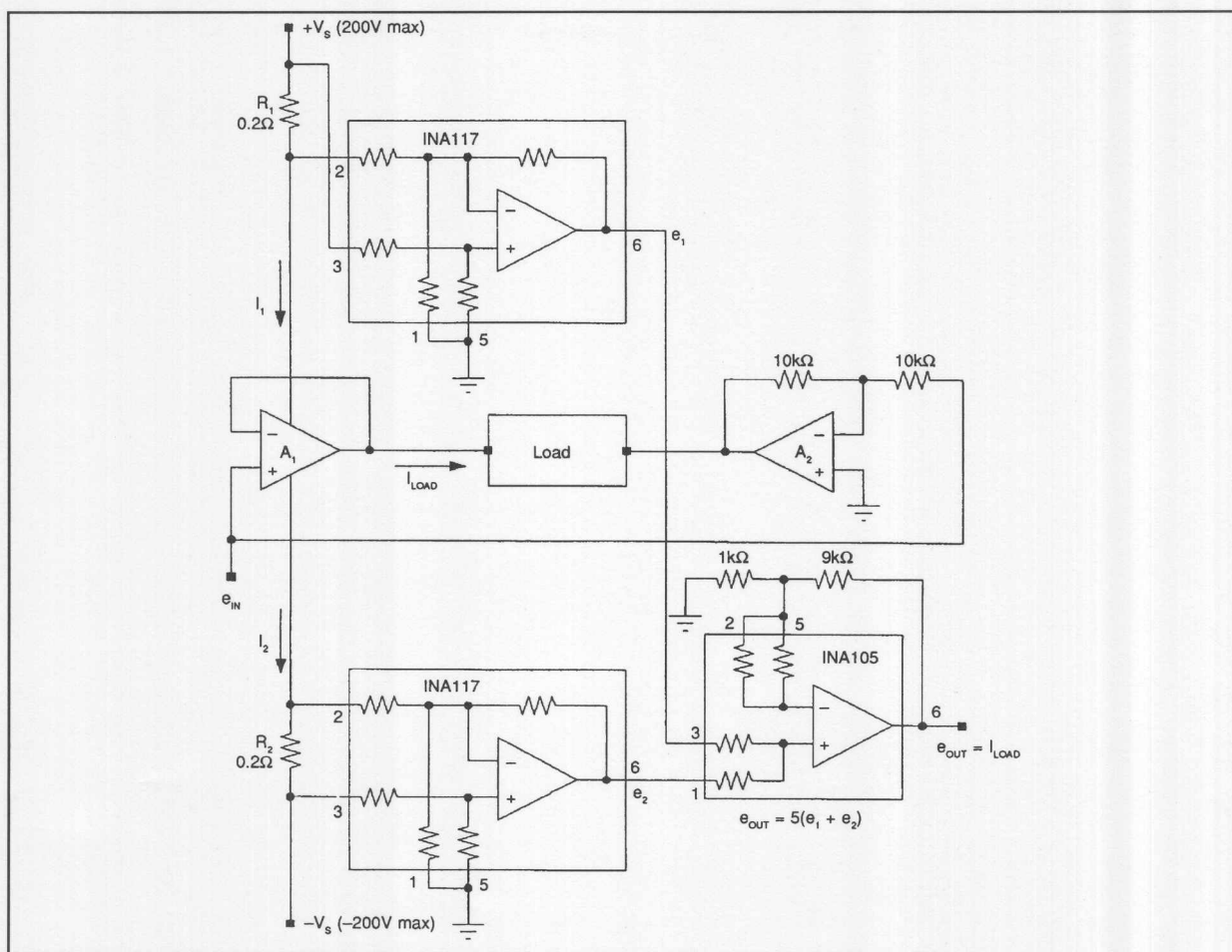


FIGURE 56. Bridge amplifier load current monitor using the INA117.

To understand how the circuit works, notice that since no current flows into the inputs of A_1 :

$$I_{LOAD} = I_1 - I_2$$

If

$$R_1 = R_2 = R$$

Then

$$e_1 = I_1 \cdot R,$$

$$e_2 = -I_2 \cdot R,$$

and

$$e_1 + e_2 = I_{LOAD} \cdot R$$

The INA105 is connected as a noninverting summing amplifier with a gain of 5 (the accurate matching of the two 25kΩ input resistors makes a very accurate summing amplifier).

Then

$$e_o = 5(e_1 + e_2) = 5(I_{LOAD} \cdot R),$$

since

$$R = 0.2\Omega,$$

$$e_o = I_{LOAD} [1V/A]$$

4 to 20mA CURRENT LOOP RECEIVER WITH 0 to 5V OUTPUT USES THE RCV420

The RCV420 is a current-to-voltage converter designed specifically for conversion of 4-20mA input currents into 0-5V outputs. A pair of precision 75Ω sense resistors are provided internally allowing both inverting and noninverting transfer functions. Input common mode signals up to ±40V can be accommodated due to the internal 4/1 input attenuator. Also, the precision 10.0V reference used for span offsetting is available to the user.

Figure 57 shows a typical application. For more details and applications, request product data sheet PDS-837.

VIRTUAL GROUND CURRENT-TO-VOLTAGE CONVERTER

When current-to-voltage conversion with no voltage burden is needed, used the transimpedance amplifier Figures 58—61. In this circuit, an op amp drives the current input node to virtual ground by forcing a current equal to I_{IN} through the feedback resistor, R_{FB} . Notice that the transfer function is inverted:

$$V_{OUT} = -I_{IN} \cdot R_{FB}$$

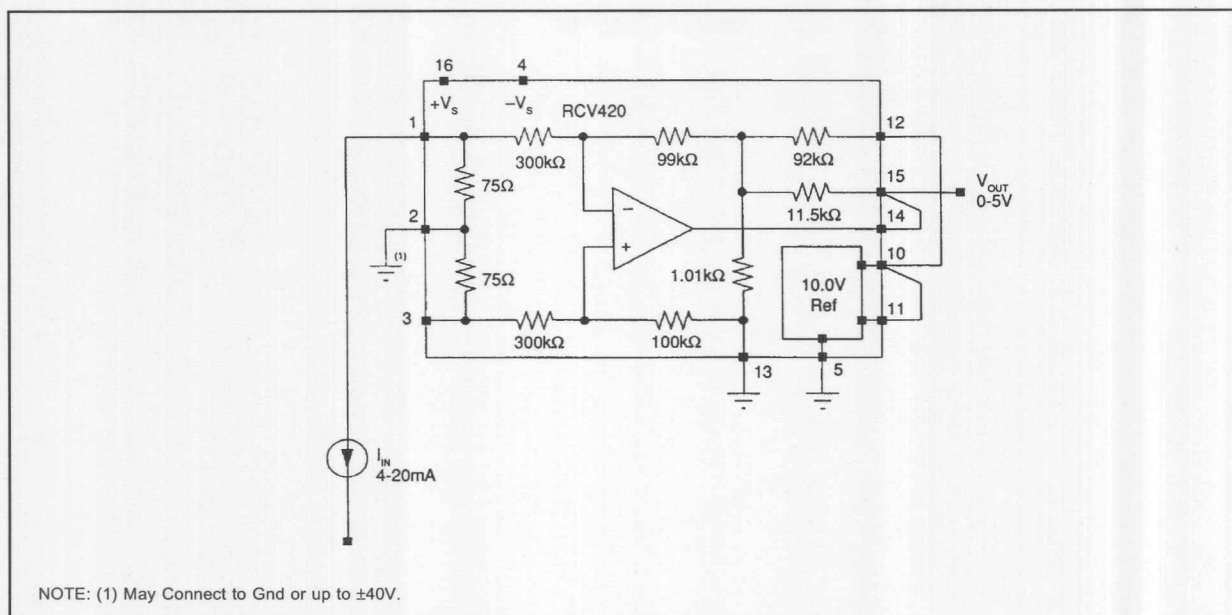


FIGURE 57. 4-20mA current loop receiver using the RCV420.

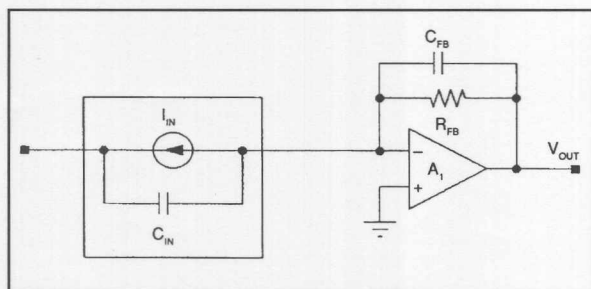


FIGURE 58. Virtual ground current-to-voltage converter.

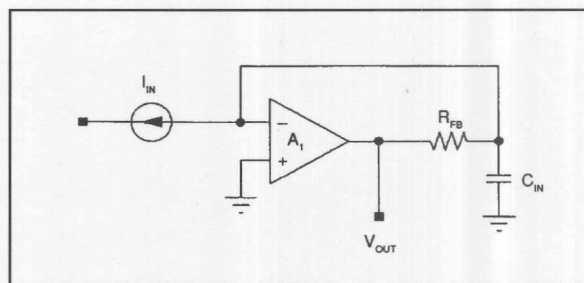


FIGURE 59. Virtual ground current-to-voltage converter redrawn to illustrate phase delay due to input capacitance and feedback resistor.

The feedback capacitor, C_{FB} , may be needed for circuit stability. To see why, consider the redrawn circuit, Figure 59. C_{IN} represents the input capacitance of the circuit and includes input source capacitance, and op amp input capacitance. Notice that R_{FB} and C_{IN} form a single pole filter in the feedback path to the op amp input. Phase delay through this circuit subtracts from the op amp phase margin which may result in instability, especially with the large values of R_{FB} often used in these circuits. If $C_{FB} \geq C_{IN}$, the phase delay will be less than 20° assuring stability with most unity-gain-stable amplifiers.

PHOTODIODE AMPLIFIER USING VIRTUAL GROUND I/V CONVERTER

The photodiode amplifier shown in Figure 60 is a common application of the transimpedance (current-to-voltage) amplifier. In this application, the shunt capacitance of the photodiode reacting with the relatively large feedback resistor creates excess noise gain. The 1pF feedback capacitor

minimizes the peaking and improves stability as discussed previously. Capacitors with the small values often required may be difficult to obtain. By using a capacitor divider circuit shown in Figure 60A, a larger value capacitor can be used. In this example, the 10pF capacitor, C_1 , is reduced to an effective value of 1pF by the R_4 , R_5 10/1 divider. The 100 pF capacitor, C_3 , keeps the Impedance of the divider low beyond the C_1 , $R_4 \parallel R_5$ zero to maintain C_1 's effect. It also produces a second-order (40dB/decade) roll-off approximately one decade beyond the $C_1/10$, R_2 pole.

The addition of two passive components to the standard configuration as shown in Figure 61 introduces a second pole that significantly reduces noise. The modification also has other advantages.

The added pole of the improved circuit is formed with R_3 and C_2 . Because the pole is placed within the feedback loop, the amplifier maintains its low output impedance. If the pole were placed outside the feedback loop, an additional buffer would be required. The extra buffer would add additional noise and DC error.

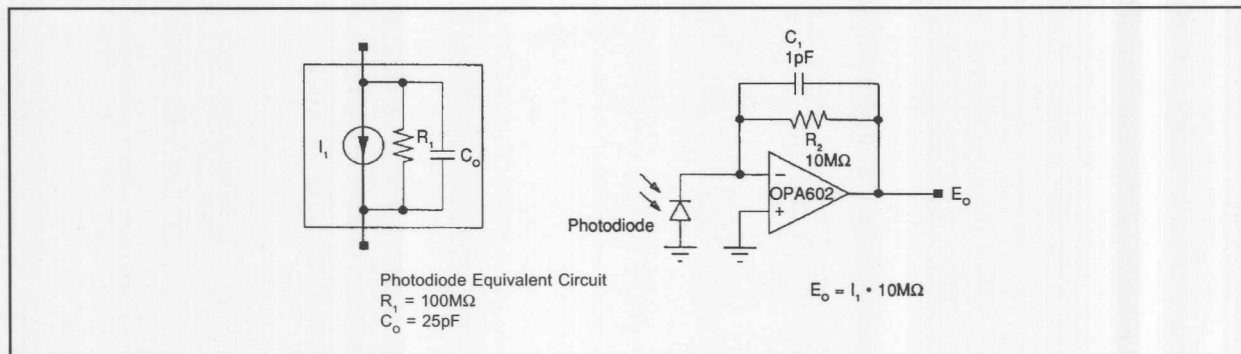


FIGURE 60. Standard transimpedance photodiode amplifier.

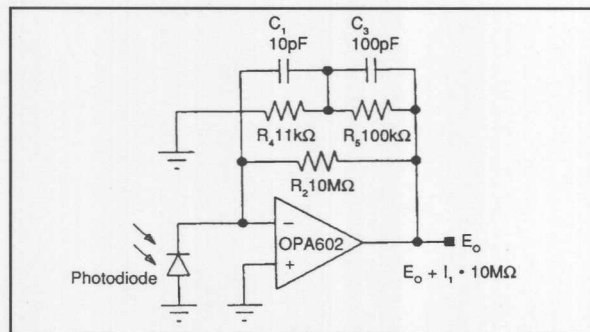


FIGURE 60A. Standard Transimpedance Amplifier with capacitor divider and added feedback pole.

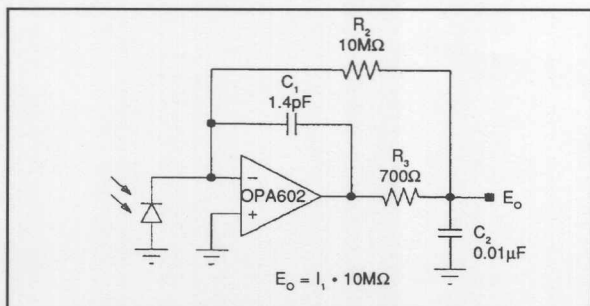


FIGURE 61. Improved transimpedance photodiode amplifier.

The signal bandwidth of both circuits is 16kHz:

$$f_{-3dB} = \frac{1}{2 \cdot \pi \cdot R_2 \cdot C_1} \text{ [Hz]} \rightarrow \text{standard circuit}$$

$$f_{-3dB} = \frac{1}{2 \cdot \pi \cdot (R_2 \cdot C_1 \cdot R_3 \cdot C_2)^{1/2}} \text{ [Hz]} \rightarrow \text{improved circuit}$$

Where, for the improved circuit:

$$C_1 \cdot R_2 = 2(C_2 \cdot R_3)$$

$$\text{and } R_2 \gg R_3$$

In the standard circuit, a single 16kHz pole is formed by the 1pF capacitance in the feedback loop. The improved circuit

exhibits two pole response. With $C_1 \cdot R_2 = 2 \cdot C_2 \cdot R_3$, the transfer function is two pole Butterworth (maximally flat in the passband). Figure 62 shows the transimpedance frequency response of the two circuits. At DC, the gain is 140dB or 10V/μA. The frequency response of both circuits is 3dB down at 16kHz. The conventional circuit rolls off at 20dB/decade, while the improved circuit rolls off at 40dB/decade.

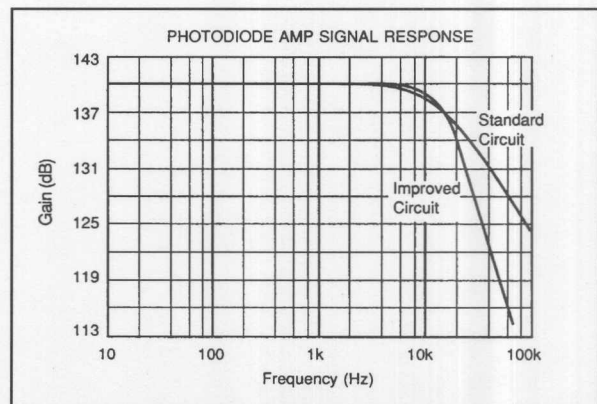


FIGURE 62. Transimpedance signal response of standard and improved photodiode amplifier.

Figure 63 shows the noise gain of both circuits. The noise problem is due to the noise gain zero formed by the relatively high photodiode shunt capacitance, C_0 , reacting with the high 10MΩ feedback resistor. The noise zero occurs at:

$$f_z = \frac{(R_1 + R_3)}{2 \cdot \pi \cdot R_1 \cdot R_3 \cdot (C_0 + C_1)} \sim 673\text{Hz in this example.}$$

Both curves show peaking in the noise gain at about 673Hz due to the zero formed by the photodiode shunt capacitance. The added pole of the improved circuit rolls off the noise gain at a lower frequency, which reduces the noise above 20kHz. Since the signal bandwidth is 16kHz, the region of the spectrum above 20kHz contains only noise, not signal. With the values shown, the improved circuit has 3 times less noise. With the OPA602 (voltage noise = 12nV/√Hz), and including resistor noise, the improved circuit has 1Hz to 100MHz noise of 68μVrms vs 205μVrms for the standard circuit.

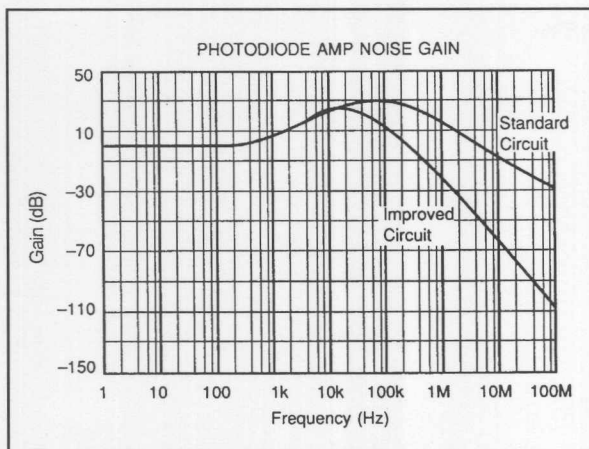


FIGURE 63. Noise gain of standard and improved photodiode amplifier.

Another advantage of the improved circuit is its ability to drive capacitive loads. Since the output of the circuit is connected to a large capacitor, C_2 , driving a little extra capacitance presents no stability problems. Although the circuit has low DC impedance, the AC transfer function is affected by load. With reasonable loads, the effect is minimal. With the values shown, a load of 10k Ω in parallel with 100pF has little effect on circuit response.

For applications where the photodiode can be floated consider the noninverting I/V converter shown in Figures 64 and 65. Notice that the buffer amplifier forces zero volts across the photodiode as in the conventional transimpedance amplifier configuration.

FET input amplifiers are commonly used for photodiode amplifier applications because of their low input bias currents. However, FET amplifier bias currents increase dramatically at high temperatures (doubling approximately every 8 to 10°C). Seemingly small input bias currents at 25°C can become intolerable at high temperature. An amplifier with only 1pA bias current at 25°C could have nearly 6nA bias current at 125°C.

The difference between input bias currents, offset current, is often much better than the absolute bias current. The typical bias current of an OPA156, for example, is 30pA, while its offset current is 3pA.

If amplifier bias current is a problem consider the circuit shown in Figure 66. The added bias current cancellation resistor R_2 cancels the effect of matching op amp input bias currents. This can provide a ten-to-one or better improvement in performance since voltage offset is due only to I_{OS} (offset current) reacting with 5M Ω .

A word of caution. Many amplifiers, especially bipolar input amplifiers, achieve low bias current with internal bias current cancellation circuitry. There may be little or no difference between their I_B and I_{OS} . In this case external bias current cancellation will not improve performance.

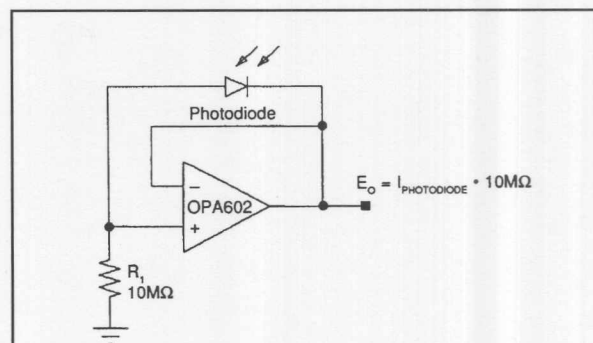


FIGURE 64.

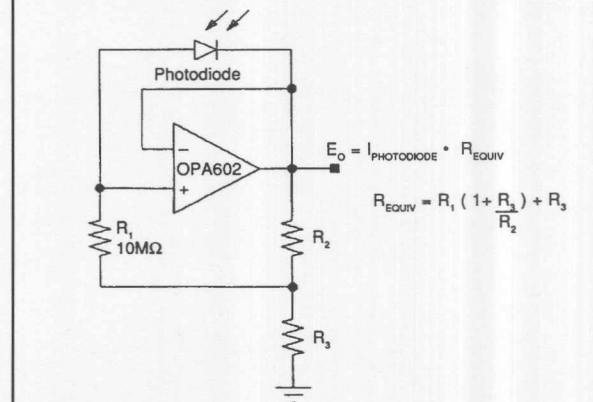


FIGURE 65.

FIGURES 64 and 65. Photodiode amplifier using floating virtual ground current-to-voltage converter.

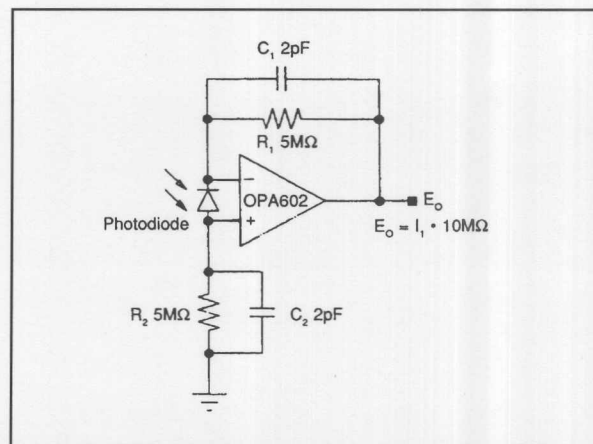


FIGURE 66. Differential Photodiode Transimpedance Amplifier gives bias current cancellation.

GLOSSARY

ABBREVIATIONS, DEFINITIONS

Bidirectional Current Source—A floating current source that provides a constant current independent of the polarity of applied voltage bias.

Current Source—This may be a general term for any current source, current sink, or floating current source. In this text it usually refers to a current generating device referenced to a positive fixed potential such as $+V_s$ of a power supply. The load must be connected between the current source and a more negative potential.

Current Sink—Current generating device referenced to a negative fixed potential such as $-V_s$ of a power supply. The load must be connected between the current sink and a more positive potential.

Difet®—Burr-Brown's trademark for an integrated circuit process which uses dielectric (DI) instead of reverse biased junctions (JI) to isolate devices. This technique eliminates the substrate leakage inherent in JI processes. The result is lower input bias currents for FET input amplifiers, and potential for higher temperature operation and radiation hardness.

Floating Current Source—A current generating device with both ends uncommitted. The load may be connected to either end, or a floating current source may be connected arbitrary between two loads. The current sources in the REF200 are floating current sources. A floating current source may require external power supplies. The floating current sources in the REF200 are self powered, and require no external power supply.

IA—Instrumentation Amplifier. An IA is not an op amp. Unlike an op amp, an IA amplifies the signal at its inputs by

a fixed gain while rejecting the common mode signal. An op amp amplifies the signal at its inputs by its open loop gain (ideally infinity). An op amp therefore requires feedback components to make a useful amplifier. It normally takes three op amps and seven precision resistors to make an IA.

I_B —Bias current. The DC current that flows into or out of the input terminals of an amplifier.

IC—Integrated circuit. Often implies monolithic integrated circuit, which is a single-chip electronic circuit.

I_{os} —Offset current. The difference in I_B of the two inputs of an amplifier.

Op Amp—Operational amplifier. An operational amplifier is a very high gain direct current amplifier with differential inputs. It is intended for applications where the transfer function is determined by external feedback components.

RTD—Resistor Temperature Device. A precision temperature transducer using platinum as the active element. Values at 0°C of 100Ω, 500Ω, and 1000Ω are standard. Due to the high cost of platinum 1kΩ RTDs are becoming more popular.

TCR—Temperature coefficient of resistance. The change of DC resistance with temperature of a resistor. Usually expressed in parts per million per °C [ppm/°C].

TCR Tracking—The match or tracking over temperature of the TCR of two or more resistors.

Transconductance Amplifier—A voltage to current converter.

Transimpedance Amplifier—A current to voltage converter. (Sometimes called transadmittance).

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.